

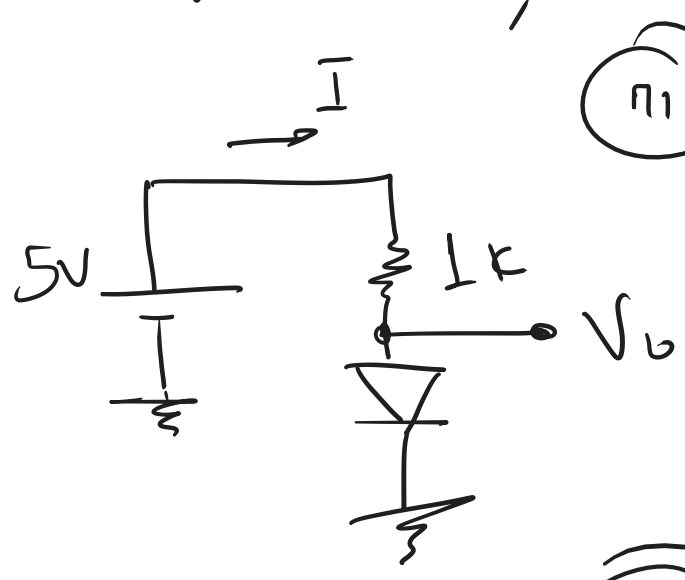
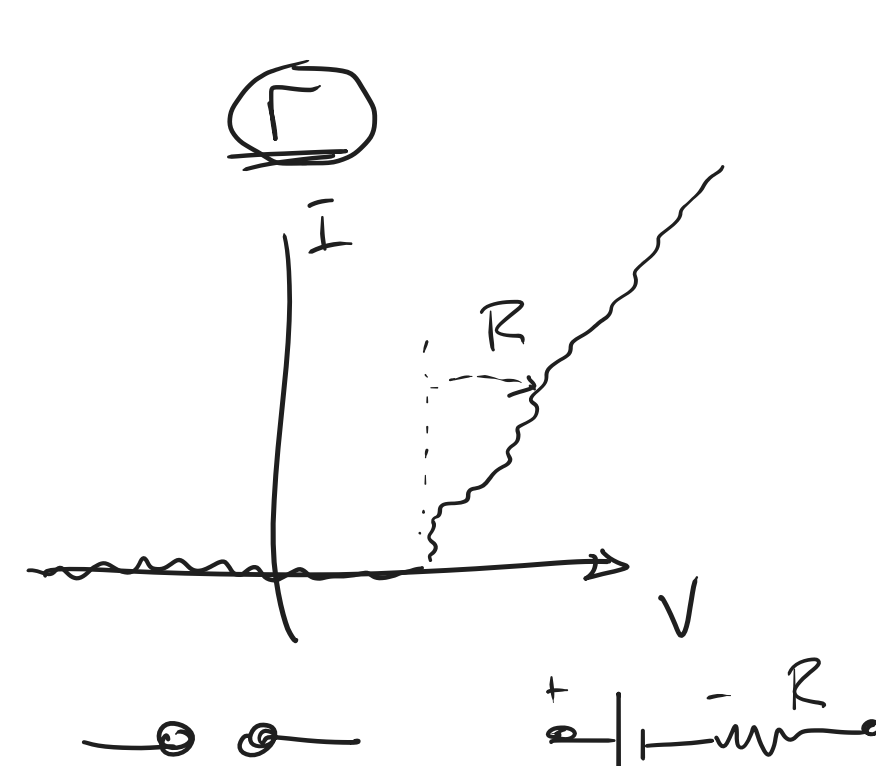
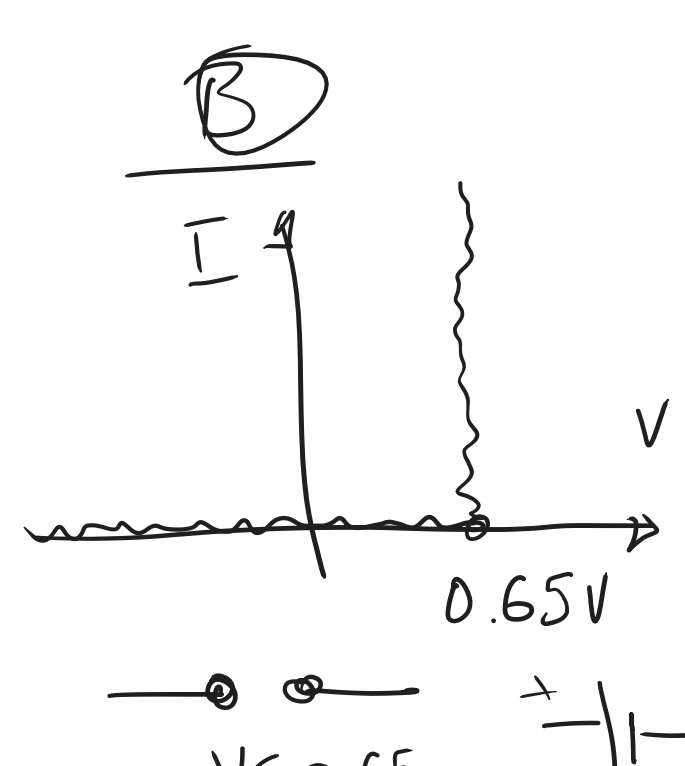
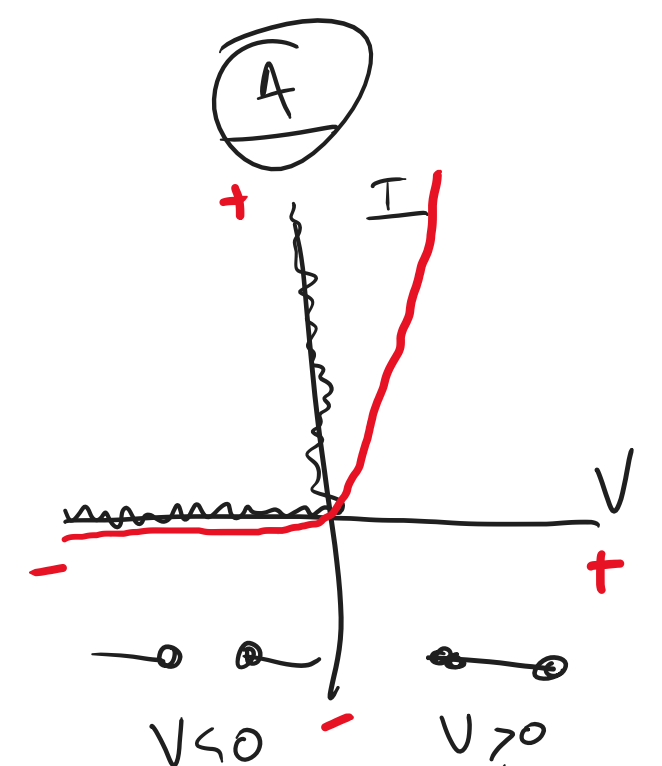


ΠΡΟΞΕΓΓΙΣΗ ΛΕΙΤΟΥΡΓΙΑΣ ΔΙΟΔΩΝ

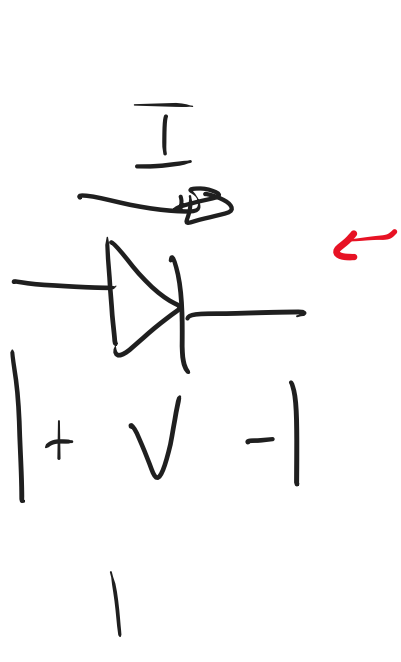


$V_0 = 0.7V = 700mV$
 $I_B = \frac{5V - 0.7V}{1k\Omega} = 4.3mA$

$I_A = \frac{5V}{1k\Omega} = 5mA$

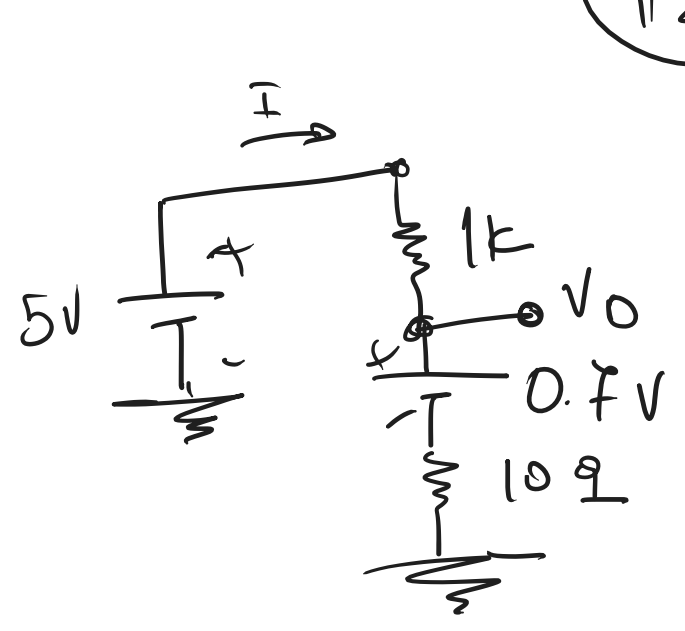



$I_f = \frac{5 - 0.7V}{1010\Omega} = \frac{4.3}{1010} = 4.257mA$

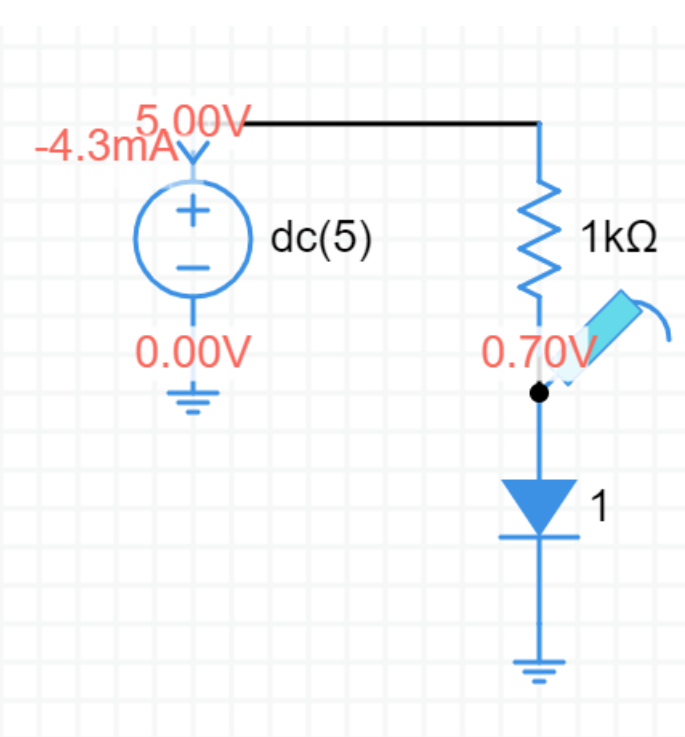$V_0 = 10\Omega \times 4.257mA + 0.7V = 42.57mV + 700mV = 742.57mV$




Edit Properties
 Name:
 Area: 1
 Is: 1.0e-14
 Vt: 0.026
 Type: normal

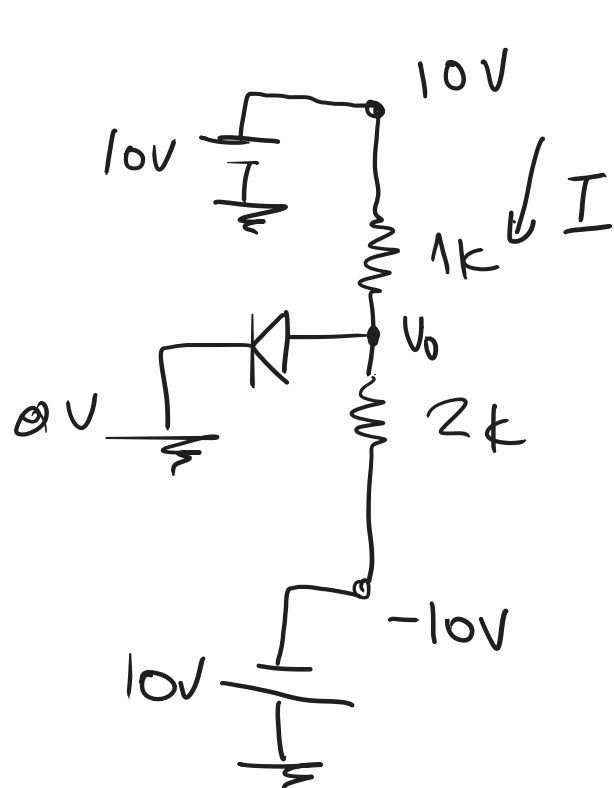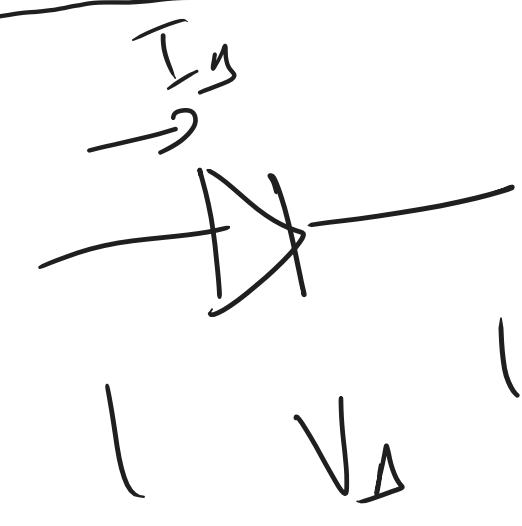$I_D = I_S \left[e^{\frac{V_D}{mV_T}} - 1 \right]$




ΕΣΤΩ ΟΤΙ $V_0 < 0V \Rightarrow$ ΤΟΤΕ ΔΙΟΔΟΣ ΑΝΑΕΤΡΩΘΑ ΠΟΛΩΜΕΝΗ

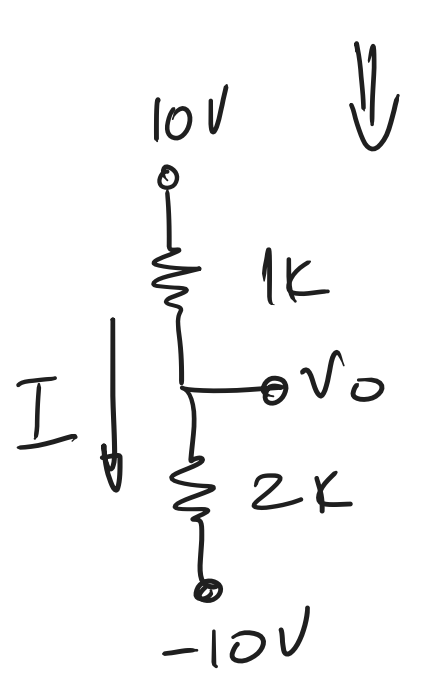$I = \frac{10V - (-10V)}{3k\Omega} = \frac{20V}{3k\Omega} = 6.6mA$



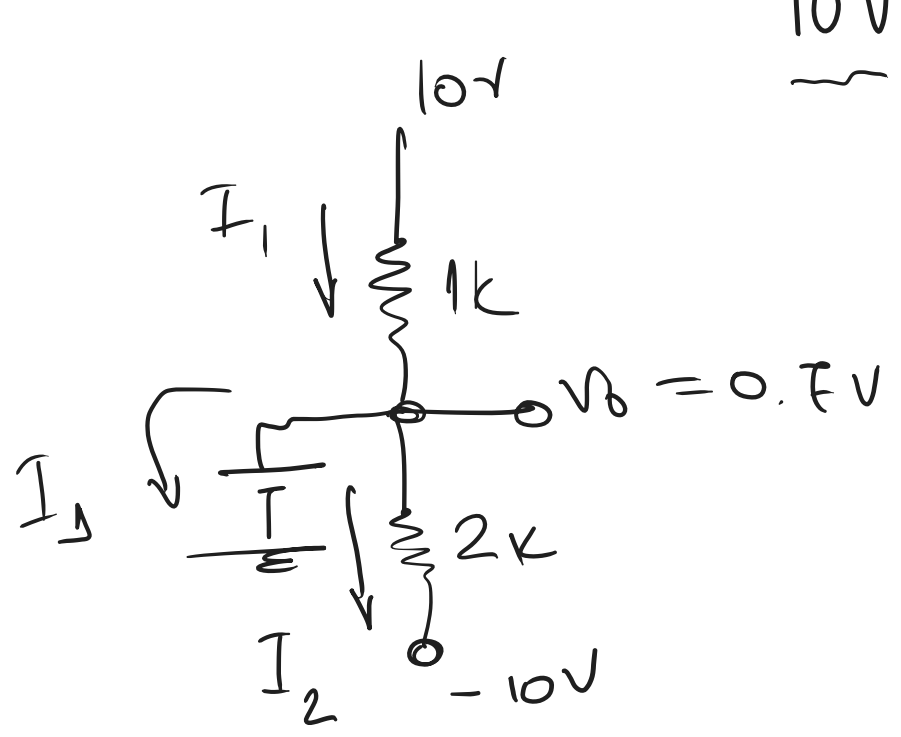$10V - 1k\Omega \times 6.6mA = 10V - 6.6V = 3.4V = V_0$




$I_1 = \frac{10V - 0.7V}{1k\Omega} = 9.3mA$

$I_D = I_1 - I_2 = 9.3 - 5.35mA$

$I_2 = \frac{0.7V - (-10V)}{2k\Omega} = \frac{10.7V}{2k\Omega} = 5.35mA$

$I_D = 3.95mA$


POWER LED

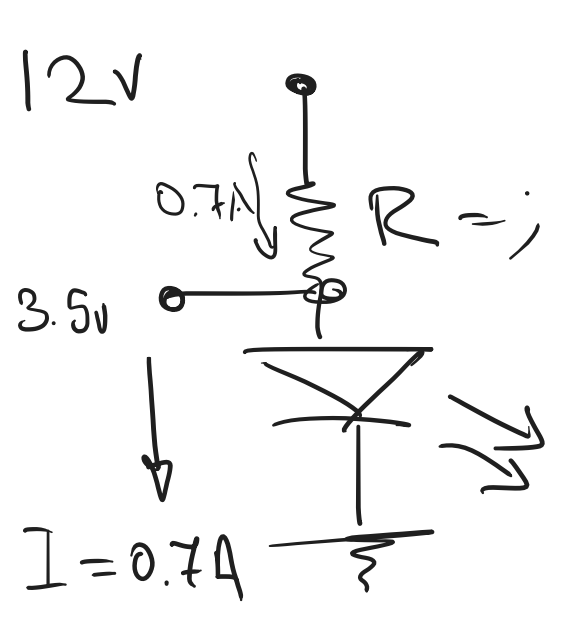

$R = \frac{12 - 3.5}{0.7} \frac{V}{A} = 12.14\Omega$

$P_R = (12 - 3.5) \cdot 0.7 = 5.95W$

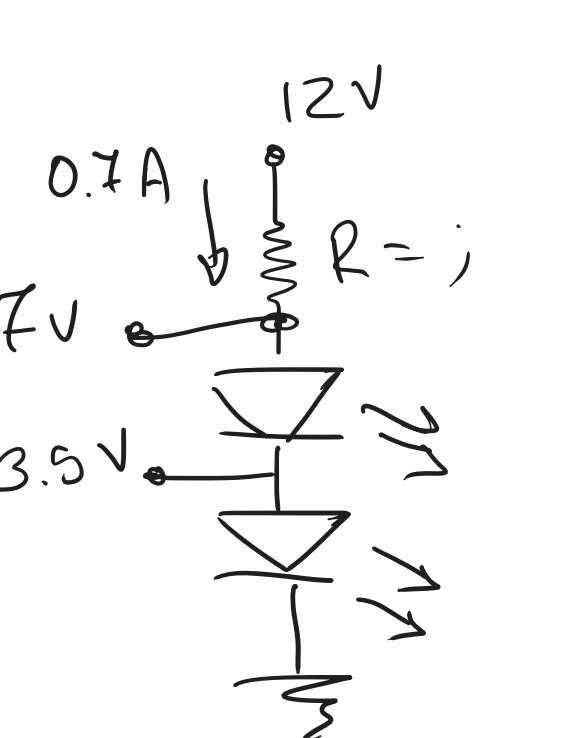
ΑΝΔΟΣΗ = $\frac{P_{\text{πΗΞΙΜΗ}}}{P_{\text{ΕΙΣΡΟΗΚΗ}}} = \frac{3.5V \times 0.7A}{12V \times 0.7A} = \frac{3.5}{12} = 29\%$



$R = \frac{12 - 7}{0.7} \frac{V}{A} = 5.7\Omega$

$P_R = (12 - 7) \times 0.7 = 3.5W$

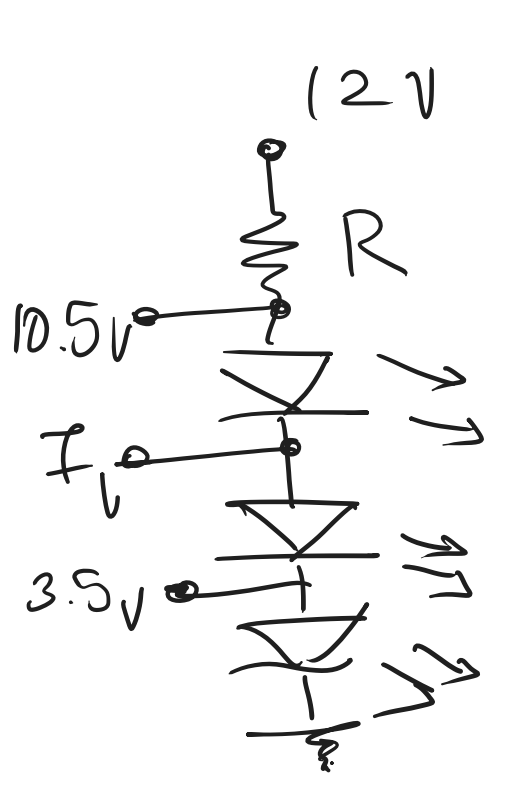
ΑΝΔΟΣΗ = $\frac{P_{\text{πΗΞΙΜΗ}}}{P_{\text{ΕΙΣΡΟΗΚΗ}}} = \frac{7V \times 0.7A}{12V \times 0.7A} = 58\%$



$R = \frac{12 - 10.5}{0.7} = 2.14\Omega$

$P_R = (12 - 10.5) \cdot 0.7 = 1.05W$

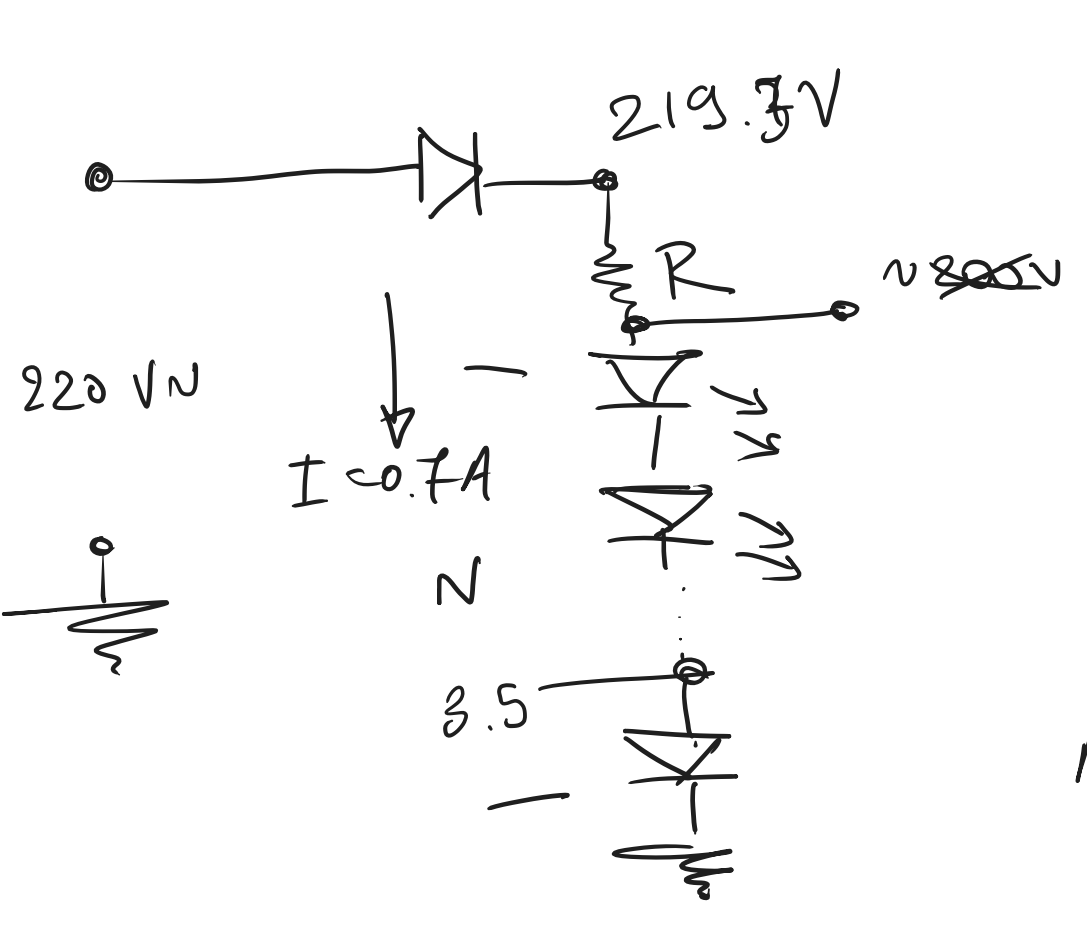ΑΝΔΟΣΗ = $\frac{P_{\text{πΗΞΙΜΗ}}}{P_{\text{ΕΙΣΡΟΗΚΗ}}} = \frac{10.5V \times 0.7A}{12V \times 0.7A} = 87.5\%$



$3.5V \times N = 200V \Rightarrow N = \frac{200}{3.5} = 57.14 \approx 58$

$58 \times 3.5V = 203V$

$R \approx \frac{220 - 203}{0.7} = 24.28\Omega$

ΑΝΔΟΣΗ = $\frac{P_{\text{πΗΞΙΜΗ}}}{P_{\text{ΕΙΣΡΟΗΚΗ}}} = \frac{203V \times 0.7A}{220V \times 0.7A} = 92.2\%$

ΔΙΟΔΟΙ \rightarrow ΑΝΟΡΘΩΣΗ ΤΑΣΗΣ