
 


# Dynamic Domino CMOS Logic

---

- One technique to help decrease power in MOS logic circuits is dynamic logic
- Dynamic logic uses different precharge and evaluation phases that are controlled by a system clock to eliminate the dc current path in single channel logic circuits
- Early MOS logic required multiphase clocks to accomplish this, but CMOS logic can be operated dynamically with a single clock




# Dynamic CMOS Logic

 

Precharge phase ( $\phi$  low)  $Q_p$  ON  
Evaluation phase ( $\phi$  high)  $Q_n$  ON
  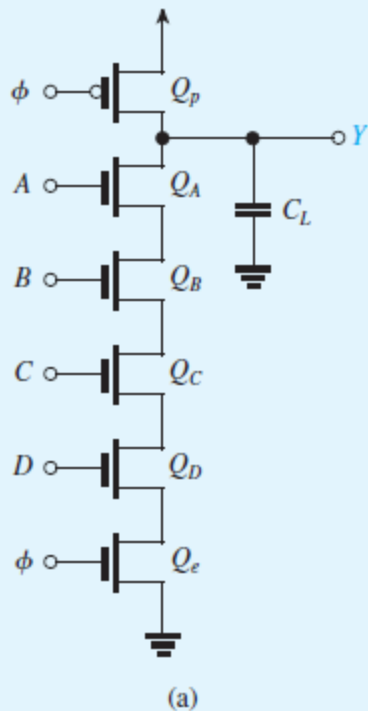
# παράδειγμα

fabricated in a 0.18- $\mu\text{m}$  CMOS technology for which  $V_{DD} = 1.8\text{ V}$ ,  $V_t = 0.5\text{ V}$ , and  $\mu_n C_{ox} = 4\mu_p C_{ox} = 300\text{ }\mu\text{A/V}^2$ . To keep  $C_L$  small, NMOS devices with  $W/L = 0.27\text{ }\mu\text{m}/0.18\text{ }\mu\text{m}$  are used (including transistor  $Q_e$ ). The PMOS precharge transistor  $Q_p$  has  $W/L = 0.54\text{ }\mu\text{m}/0.18\text{ }\mu\text{m}$ . The total capacitance  $C_T$  is found to be 20 fF.



# παράδειγμα

$$\begin{aligned}i_{D(0.1V_{DD})} &= \frac{1}{2}\mu_p C_{ox}\left(\frac{W}{L}\right)_p (V_{DD} - |V_{tp}|)^2 \\&= \frac{1}{2} \times 75 \times \frac{0.54}{0.18} (1.8 - 0.5)^2 \\&= 190.1 \mu\text{A}\end{aligned}$$

$$\begin{aligned}i_{D(0.9V_{DD})} &= \mu_p C_{ox}\left(\frac{W}{L}\right)_p \left[ (V_{DD} - |V_{tp}|)(V_{DD} - 0.9V_{DD}) - \frac{1}{2}(V_{DD} - 0.9V_{DD})^2 \right] \\&= 75 \times \frac{0.54}{0.18} \left[ (1.8 - 0.5)(1.8 - 1.62) - \frac{1}{2}(1.8 - 1.62)^2 \right] \\&= 49 \mu\text{A}\end{aligned}$$

$$\begin{aligned}t_r &= \frac{C\Delta v_T}{I_{av}} \\&= \frac{C(0.9V_{DD} - 0.1V_{DD})}{I_{av}} \\t_r &= \frac{20 \times 10^{-15} \times 0.8 \times 1.8}{119.6 \times 10^{-6}} = 0.19 \text{ ns}\end{aligned}$$

# παράδειγμα

A=B=C=D=1 (evaluation)

$$\begin{aligned}i_D(V_{DD}) &= \frac{1}{2}(\mu_n C_{ox})\left(\frac{W}{L}\right)_{\text{eq}} (V_{DD} - V_t)^2 \\&= \frac{1}{2} \times 300 \times 0.3 (1.8 - 0.5)^2 \\&= 76.1 \mu\text{A}\end{aligned}$$


At  $v_I = V_{DD}/2$ ,  $Q_{\text{eq}}$  will be operating in the triode region; thus,

$$\begin{aligned}i_D(V_{DD}/2) &= (\mu_n C_{ox})\left(\frac{W}{L}\right)_{\text{eq}} \left[ (V_{DD} - V_t) \frac{V_{DD}}{2} - \frac{1}{2} \left( \frac{V_{DD}}{2} \right)^2 \right] \\&= 300 \times 0.3 \left[ (1.8 - 0.5) \left( \frac{1.8}{2} \right) - \frac{1}{2} \left( \frac{1.8}{2} \right)^2 \right] \\&= 68.9 \mu\text{A}\end{aligned}$$

$$\begin{aligned}t_{PHL} &= \frac{C(V_{DD} - V_{DD}/2)}{I_{\text{av}}} \\&= \frac{20 \times 10^{-15} (1.8 - 0.9)}{72.5 \times 10^{-6}} = 0.25 \text{ ns}\end{aligned}$$

# Cascading Dynamic Logic gates


---


 


With A high, at evaluation phase  $Q1$  turns on discharging  $C_{L1}$  and **simultaneously**  $Q2$  turns on discharging  $C_{L2} \rightarrow$  ανεπιθύμητο διότι  $V_{Y2}$  πρέπει να είναι  $V_{DD}$
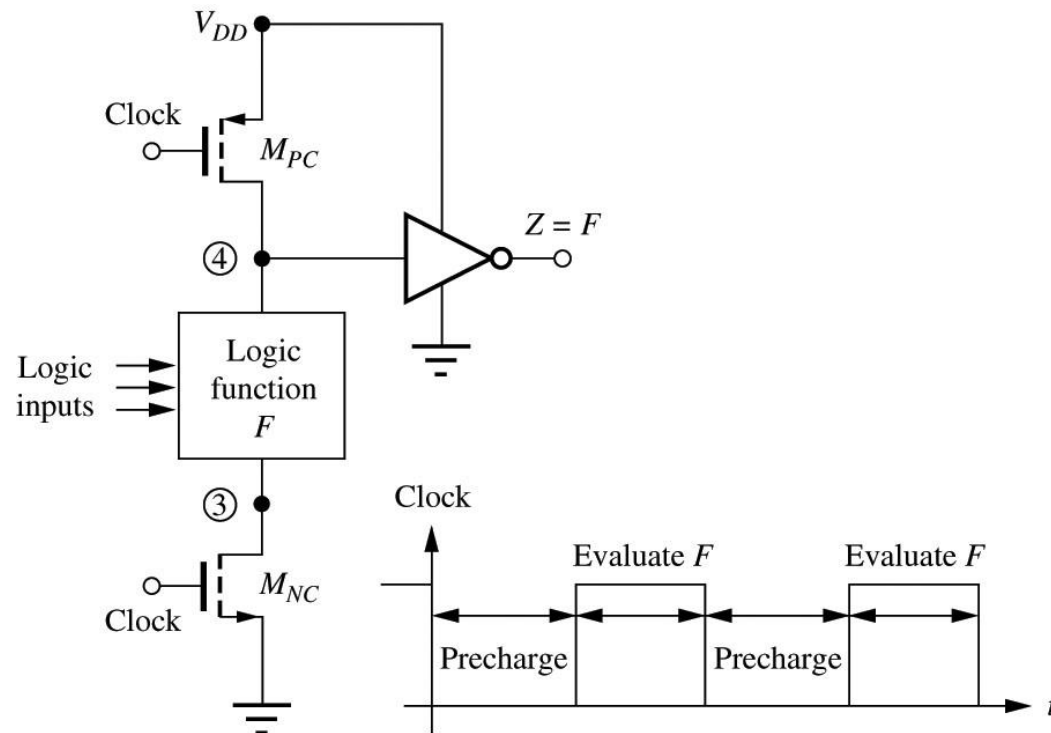
# Dynamic Domino CMOS Logic

- The figure demonstrates the basic concept of domino CMOS logic operation



 
 


(b)

(a)




# Domino CMOS Logic gates in cascade

  

Επειδή η έξοδος της πύλης Domino είναι low στην αρχή του evaluation, δεν γίνεται πρόωρη εκφόρτιση του  $C_{L2}$  στην επόμενη βαθμίδα

 
# Dynamic Domino CMOS Logic

- It should be noted that domino CMOS circuits only produce true logic outputs, but this problem can be overcome by using registers that have both true and complemented outputs to complete the function shown by the following


 
# Cascade Buffers

- In some circuits, the logic must be able to drive large capacitances (10 to 50 pF)
- By cascading a number of increasingly larger inverters, it is possible to drive the loads



# Cascade Buffers

---

- The taper factor  $\beta$  determines the increase of the cascaded inverter's size in manner shown of the previous image.

$$\beta^N = \frac{C_L}{C_o}$$

where  $C_o$  is the unit inverter's load capacitance

- The delay of the cascaded buffer is given by the following:

$$\tau_B = N \left( \frac{C_L}{C_o} \right)^{1/N} \tau_o \quad \text{where } \tau_o \text{ is the unit inverter's propagation delay}$$

# Optimum Design of Cascaded Stages

---

- The following expressions can aid in the design of an optimum cascaded buffer

$$N_{opt} = \ln\left(\frac{C_L}{C_o}\right)$$

$$\beta_{opt} = \left(\frac{C_L}{C_o}\right)^{\frac{1}{\ln\left(\frac{C_L}{C_o}\right)}} = \varepsilon$$

$$\tau_{Bopt} = \ln\left(\frac{C_L}{C_o}\right) \varepsilon \tau_o$$

# παράδειγμα

---

$C_L = 50 \text{ pF}$ ; technology has  $C_o = 50 \text{ fF}$ .

**Analysis:** The optimum value of  $N$  is  $N_{\text{opt}} = \ln C_L / C_o = \ln(1000) = 6.91$ , and the optimum delay is  $\tau_{B\text{opt}} = 6.91 \times (2.72) \times t_o = 18.8t_o$ .  $N$  must be an integer, but either  $N = 6$  or  $N = 7$

$$N = 6: \quad \tau_B = 6(1000^{1/6})\tau_o = 19.0\tau_o$$


$$N = 7: \quad \tau_B = 7(1000^{1/7})\tau_o = 18.8\tau_o$$

$$\beta = \left(\frac{C_L}{C_o}\right)^{1/N} = \left(\frac{50 \text{ pF}}{50 \text{ fF}}\right)^{1/6} = (1000)^{1/6} = \sqrt[6]{1000} = 3.16$$

$$\tau_o \cong \frac{2.4C}{K_n(V_{DD} - V_{TN})} = \frac{2.4(50 \text{ fF})}{2(100 \mu\text{A/V}^2)(3.3 - 0.75)} = 0.24 \text{ ns}$$


and the estimated buffer delay is  $\tau_B = 4.5 \text{ ns}$ .

# Pass Transistor Logic (PTL)

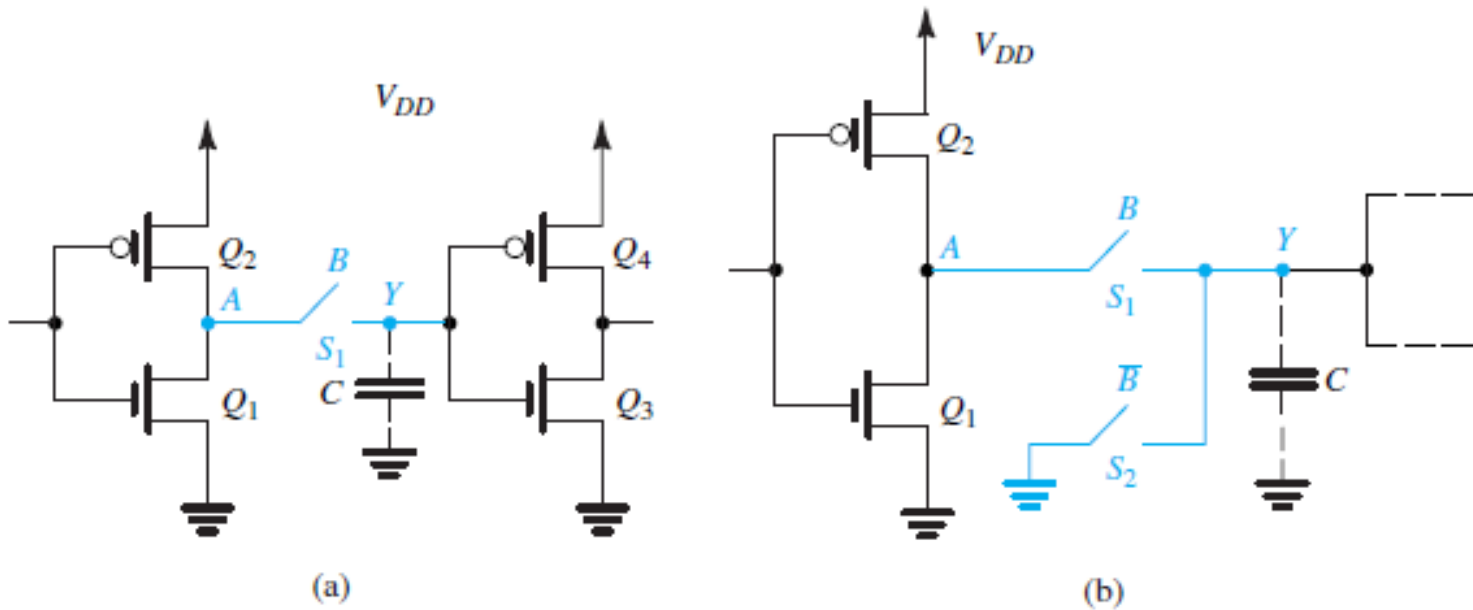

- (a) Δεν υπάρχει Low resistance path  
(b) Η διάταξη έχει Low resistance path

# Pass Transistor Logic (PTL)- II

 



# Παράδειγμα (I)

$$\mu_n C_{ox} = 50 \text{ } \mu\text{A/V}^2, \mu_p C_{ox} = 20 \text{ } \mu\text{A/V}^2, |V_{t0}| = 1 \text{ V}, \gamma = 0.5 \text{ V}^{1/2}, 2\phi_f = 0.6 \text{ V},$$

$$(W/L)_n = 2/1, (W/L)_p = 5/1$$

$$V_{OH} = V_{DD} - V_t$$

where  $V_t$  is the value of the threshold voltage at a source-body reverse bias equal to  $V_{OH}$ . Using Eq. (14.21), we have

$$\begin{aligned} V_t &= V_{t0} + \gamma (\sqrt{V_{OH} + 2\phi_f} - \sqrt{2\phi_f}) \\ &= V_{t0} + \gamma (\sqrt{V_{DD} - V_t + 2\phi_f} - \sqrt{2\phi_f}) \end{aligned}$$

$$V_t = 1.6 \text{ V}$$

$$V_{OH} = 3.4 \text{ V}$$

## Παράδειγμα (II)

---

$$i_D(0) = \frac{1}{2} \times 50 \times \frac{4}{2} \times (5 - 1)^2 = 800 \mu\text{A}$$

$$V_t \text{ (at } v_O = 2.5 \text{ V)} = 1 + 0.5(\sqrt{2.5 + 0.6} - \sqrt{0.6}) = 1.49 \text{ V}$$

$$i_D(t_{PLH}) = \frac{1}{2} \times 50 \times \frac{4}{2} (5 - 2.5 - 1.49)^2 = 50 \mu\text{A}$$

$$i_D|_{av} = \frac{800 + 50}{2} = 425 \mu\text{A}$$

$$\begin{aligned} t_{PLH} &= \frac{C(V_{DD}/2)}{i_D|_{av}} \\ &= \frac{50 \times 10^{-15} \times 2.5}{425 \times 10^{-6}} = 0.29 \text{ ns} \end{aligned}$$

## Παράδειγμα (III)

---

$$i_D(0) = \frac{1}{2} \times 50 \times \frac{4}{2} (5 - 1)^2 = 800 \mu\text{A}$$

$$\begin{aligned} i_D(t_{PHL}) &= 50 \times \frac{4}{2} \left[ (5 - 1) \times 2.5 - \frac{1}{2} \times 2.5^2 \right] \\ &= 690 \mu\text{A} \end{aligned}$$


$$i_D|_{av} = \frac{1}{2} (800 + 690) = 740 \mu\text{A}$$

$$t_{PHL} = \frac{50 \times 10^{-15} \times 2.5}{740 \times 10^{-6}} = 0.17 \text{ ns}$$



$$t_P = \frac{1}{2} (t_{PLH} + t_{PHL}) = \frac{1}{2} (0.29 + 0.17) = 0.23 \text{ ns}$$

# Υλοποίηση Διακοπών με CMOS Transmission Gate

---

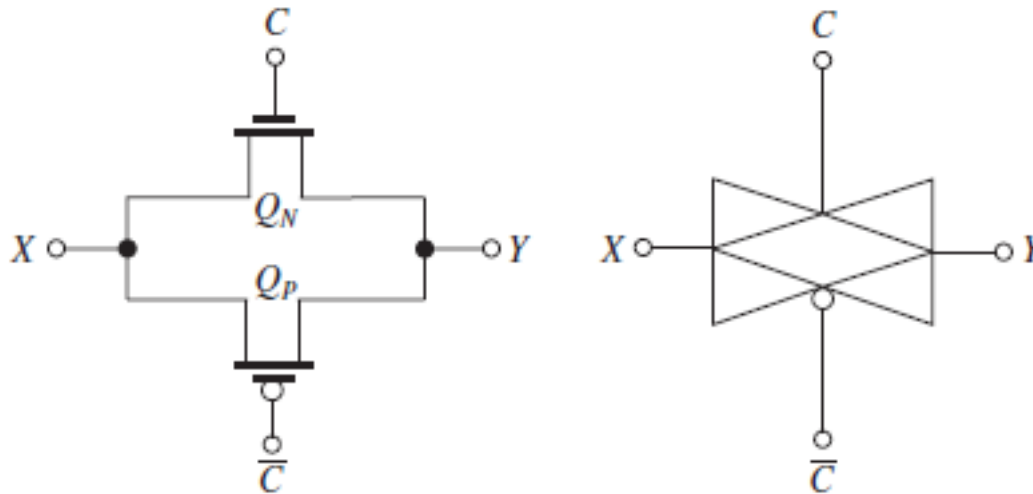

# Λειτουργία Transmission gate (I)

  

# Λειτουργία Transmission gate (II)

---

Κύκλωμα (α)

$$i_{DN} = \frac{1}{2}k_n(V_{DD} - v_O - V_{tn})^2$$

$$V_{tn} = V_{t0} + \gamma(\sqrt{v_O + 2\phi_f} - \sqrt{2\phi_f})$$

$Q_N$  will conduct a diminishing current that reduces to zero at  $v_O = V_{DD} - V_{tn}$ .

Το  $Q_P$  όμως θα συνεχίσει να άγει μέχρι να φορτιστεί πλήρως ο πυκνωτής και  $V_O = V_H = V_{DD}$ .  
Το PMOS δίνει στην πύλη ένα "καλό 1"

# Ισοδύναμη αντίσταση μιας Transmission gate

---

$$i_{DN} = \frac{1}{2}k_n(V_{DD} - V_{tn} - v_O)^2 \quad \text{for } v_O \leq V_{DD} - V_{tn}$$

$$i_{DN} = 0 \quad \text{for } v_O \geq V_{DD} - V_{tn}$$

$$R_{Neq} = \frac{V_{DD} - v_O}{\frac{1}{2}k_n(V_{DD} - V_{tn} - v_O)^2} \quad \text{for } v_O \leq V_{DD} - V_{tn}$$

$$R_{Neq} = \infty \quad \text{for } v_O \geq V_{DD} - V_{tn}$$


$$i_{DP} = \frac{1}{2}k_p(V_{DD} - |V_{tp}|)^2 \quad \text{for } v_O \leq |V_{tp}|$$

$$i_{DP} = k_p \left[ (V_{DD} - |V_{tp}|)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right] \quad \text{for } v_O \geq |V_{tp}|$$

$$R_{Peq} = \frac{V_{DD} - v_O}{\frac{1}{2}k_p(V_{DD} - |V_{tp}|)^2} \quad \text{for } v_O \leq |V_{tp}|$$

$$R_{Peq} = \frac{1}{k_p \left[ V_{DD} - |V_{tp}| - \frac{1}{2}(V_{DD} - v_O) \right]} \quad \text{for } v_O \geq |V_{tp}|$$


 
# Ισοδύναμη αντίσταση μιας Transmission gate



$$R_{TG} = R_{Neq} \parallel R_{Peq}$$



# The CMOS Transmission Gate

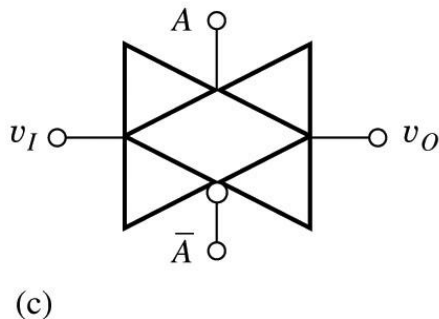 

- The CMOS transmission gate (T-gate) is a useful circuits for both analog and digital applications
- It acts as a switch that can operate up to  $V_{DD}$  and down to  $V_{SS}$

# The CMOS Transmission Gate

- The main consideration that needs to be considered is the equivalent on-resistance which is given by the following expression:

$$R_{EQ} = \frac{R_{onp} R_{onn}}{R_{onp} + R_{onn}}$$

