 


# Retiming


---

Vassilis Paliouras, Integrated System Design , ECE Dept, U. Patras



(a)
 
$$\begin{aligned}
 w(n) &= ay(n-1) + by(n-2) \\
 y(n) &= w(n-1) + x(n) \\
 &= ay(n-2) + by(n-3) + x(n).
 \end{aligned}$$




(b)

$$\begin{aligned}
 w_1(n) &= ay(n-1) \\
 w_2(n) &= by(n-2) \\
 y(n) &= w_1(n-1) + w_2(n-1) + x(n) \\
 &= ay(n-2) + by(n-3) + x(n).
 \end{aligned}$$

 
# Retiming


Moving around existing delays

- Does not alter the latency of the system
- Reduces the critical path of the system
- Node Retiming




- Cutset Retiming

 


 


(a)

 


(b)

 

(a)

 

(b)


 


(c)

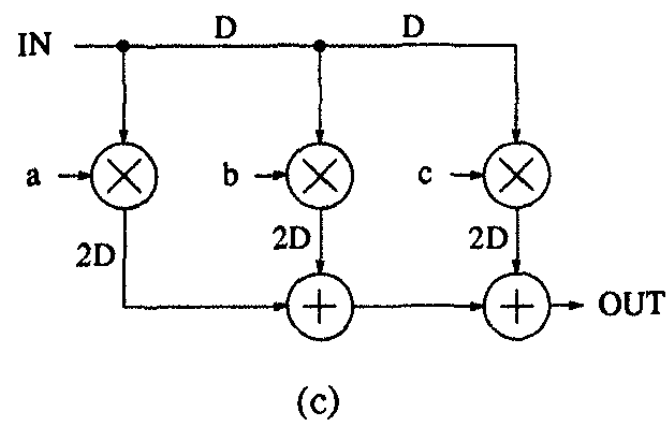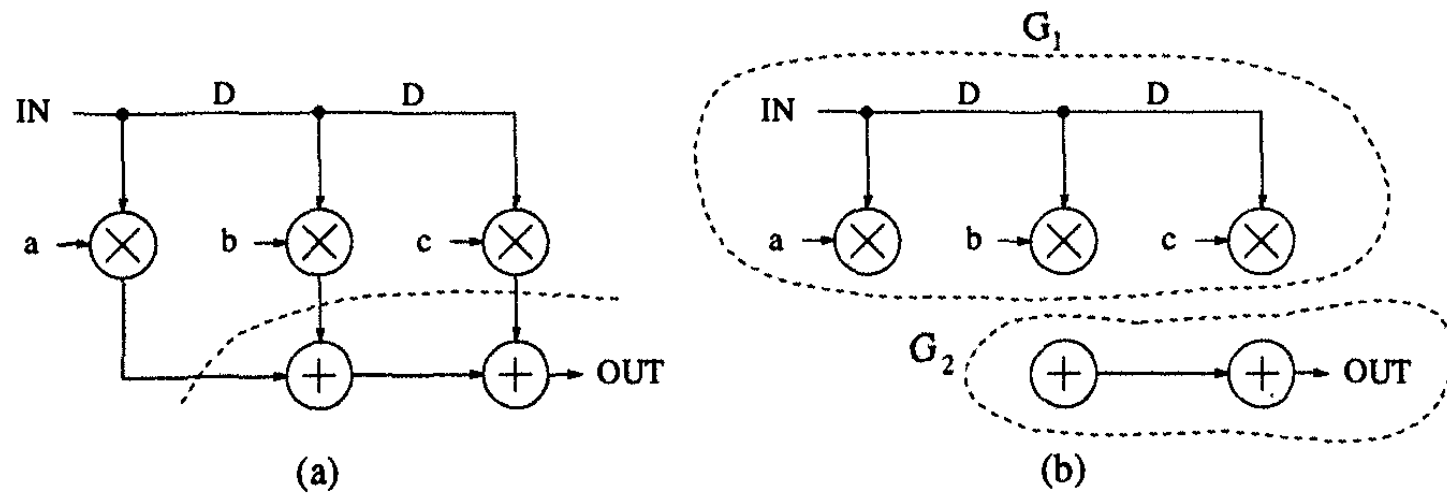
# Retiming and pipelining

Generalization of  
pipelining

Pipelining is equivalent  
to introducing many  
delays at the input  
followed by retiming



# Retiming Formulation

 

- Properties of retiming
  - The weight of the retimed path  $p = V_0 \rightarrow V_1 \rightarrow \dots \rightarrow V_k$  is given by  $\omega_r(p) = \omega(p) + r(V_k) - r(V_0)$
  - Retiming does not change the number of delays in a cycle.
  - Retiming does not alter the iteration bound in a DFG
  - Adding the constant value  $j$  to the retiming value of each node does not alter the number of delays in the edges of the retimed graph.
- Retiming is done to meet the following
  - Clock period minimization
  - Register minimization
  - Reduce power consumption



# Solving a system of inequalities


- Given  $M$  inequalities in  $N$  variables, where each inequality is of the form  $r_i - r_j \leq k$ , for integer values of  $k$ : **Use a shortest path algorithm:**
  - Draw a constraint graph
    - Draw a node  $i$  for each of the  $N$  variables  $r_i, i = 1, 2, \dots, N$ .
    - Draw a node  $N + 1$ .
    - For each inequality  $r_i - r_j \leq k$ , draw the edge  $j \rightarrow i$  of length  $k$ .
    - For each node  $i, i = 1, 2, \dots, N$ , draw the edge  $N + 1 \rightarrow i$  from the node  $N + 1$  to node  $i$  with length 0.
  - Solve using a shortest path algorithm.
    - The system of inequalities **has a solution**, iff the constraint graph contains **no negative cycles**.
    - If a solution exists, one solution is where  $r_i$  is the minimum-length path from the node  $N + 1$  to node  $i$ .

$$r_1 - r_2 \leq 3$$

$$r_3 - r_4 \leq 0$$

$$r_2 - r_3 \leq 1$$

$$r_1 - r_4 \leq -1$$

 


- Solution exists when nonnegative cycles
- Solve shortest path problem from root to every node

Solve systems of inequalities
 
# Παράδειγμα


$$\begin{aligned}r_1 - r_2 &\leq 0 \\r_3 - r_1 &\leq 5 \\r_4 - r_1 &\leq 4 \\r_4 - r_3 &\leq -1 \\r_3 - r_2 &\leq 2.\end{aligned}$$

$$\mathbf{R}^{(6)} = \begin{bmatrix} \infty & \infty & 5 & 4 & \infty \\ 0 & \infty & 2 & 1 & \infty \\ \infty & \infty & \infty & -1 & \infty \\ \infty & \infty & \infty & \infty & \infty \\ 0 & 0 & 0 & -1 & \infty \end{bmatrix}$$


 
# Retiming for Clock Period Minimization

- **Feasibility constraint:** forces the number of delays on each edge of the retimed graph to be non negative
  - $\omega'(U, V) \geq 0$  causality of the system
  - $\omega'(U, V) \geq r(U) - r(V)$  (one inequality per edge)
- **Critical Path constraint:** enforces that the minimum feasible clock period  $\Phi(G)$  is less than the target clock period  $c$ 
  - Define two quantities  $W(U, V)$  and  $D(U, V)$  as:
    - $W(U, V) = \min\{w(p): U \rightarrow V\}$
    - $D(U, V) = \max\{t(p): U \rightarrow V \text{ and } w(p) = W(U, V)\}$
- Then it should hold that  $r(U) - r(V) \leq W(U, V) - 1$ , for all vertices  $U$  and  $V$  in the graph, for which  $D(U, V) > c$ .




Namely: For those paths for which the computation time exceeds the target clock period  $c$ , we demand that they are not critical paths (their retimed version contains at least 1 delay)

$$W(A, E) = 1 \quad \& \quad D(A, E) = 5$$
 
# Algorithm to compute $W(U, V)$ and $D(U, V)$

- Let  $M = t_{\max}n$ , where  $t_{\max}$  is the maximum computation time of the nodes in  $G$  and  $n$  is the # of nodes in  $G$ .
- Form a new graph  $G'$  which is the same as  $G$  except the edge weights are replaced by  $w'(e) = Mw(e) - t(U)$ , for all edges  $e: U \rightarrow V$ .
- Solve for all-pairs shortest path problem on  $G'$  by using Floyd-Warshall algorithm. Let  $S'_{UV}$  be the shortest path from  $U \rightarrow V$ .
- If  $U \neq V$ , then
  - $W(U, V) = \left\lceil \frac{S'_{UV}}{M} \right\rceil$  and
  - $D(U, V) = MW(U, V) - S'_{UV} + t(V)$ .
- If  $U = V$ , then  $W(U, V) = 0$  and  $D(U, V) = t(U)$ .
- Using  $W(U, V)$  and  $D(U, V)$ , the **feasibility** and **critical path** constraints are formulated to give certain inequalities.
- The inequalities are solved using constraint graphs, and, ***if a feasible solution is obtained***, then the circuit can be clocked with a period  $c$ .



$$M = nt_{\max}$$


$$e : U \rightarrow V$$

$$w'(e) = Mw(e) - t(U)$$

$$n = 4$$

$$t_{\max} = 2$$

$$M = 8$$

 

# Cutset retiming


- Special case of retiming: A graphical method that simplifies complex retiming
- Only affects the weights of the cutset edges
- Add  $k$  delays to graph  $G_1$  – remove  $k$  delays from other graph  $G_2$
- Each node in  $G_1$  has a retiming value  $j$  and each node in  $G_2$  has  $j + k$
- Pipelining is a special case of cutset retiming (and of retiming):
  - No edges in cutset that go from  $G_2$  to  $G_1$  (feed forward cutsets)
- **Cutset retiming** is often used in combination with slow down:
  - each delay is replaced with  $N$  delays to create an  $N$ -slow version of the DFG.  
Note that  $N - 1$  null operations must be interleaved after each useful signal sample to preserve the functionality.

A 100-stage **Lattice Filter** (Fig. 4.7)

**Critical path:** 2 mults and 101 adds.


Assume  $T_m = 2$  ut and  $T_a = 1$  ut

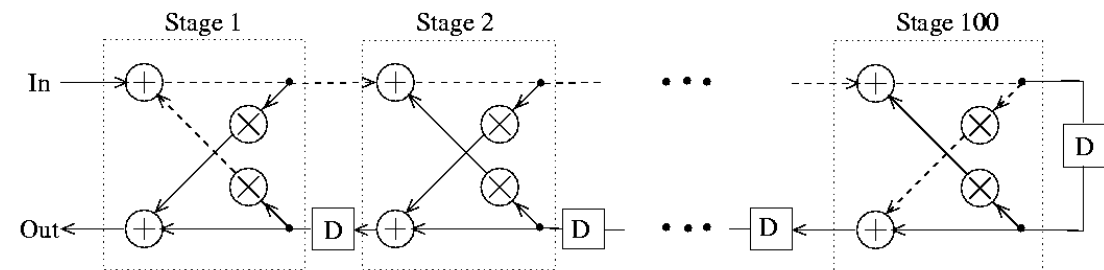➔  $T_{\text{sample}} = T_{\text{clk}} = 105$  ut






 A 2-slow version of the circuit ( $T_{\text{clk}} = 105 \text{ u.t.}$ )  
(Input new samples every alternate cycle )




 - A (cutset) retimed version of the 2-slow circuit ( $T_{\text{clk}} = 6 \text{ ut}$ )
- **Critical path:** 2 multiplications and 2 additions  
 $\rightarrow T_{\text{sample}} = 2 \times 6 = 12 \text{ ut}$


 
# $k$ -slow transformation

- Replace each  $D$  by  $kD$
- After 2-slow transformation



Clock	
0	A0→B0
1	A1→B1
2	A2→B2

$$T_{\text{iter}} = 2 \text{ ut}$$

Clock	
0	A0→B0
1	
2	A1→B1
3	
4	A2→B2


$$T_{\text{clk}} = 2 \text{ ut}$$

$$T_{\text{iter}} = 2 \times 2 = 4 \text{ ut}$$




- Input new samples every alternate cycles.
- Null operations account for odd clock cycles.
- Hardware utilized only 50% time
 
# Retiming a 2-slow graph

- $T_{\text{clk}} = 1 \text{ ut}$
- $T_{\text{iter}} = 2 \times 1 = 2 \text{ ut}$
- Hardware Utilization = 50 %
- Hardware can be fully utilized if two independent operations are available.



# Μετασχηματισμός N-slow

   

# Other Applications of Retiming

- Retiming for Register Minimization (Section 4.4.3)
- Retiming for Folding (Chapter 6)
- Retiming for Power Reduction (Chap. 17)
- Retiming for Logic Synthesis (Beyond Scope of This Class)