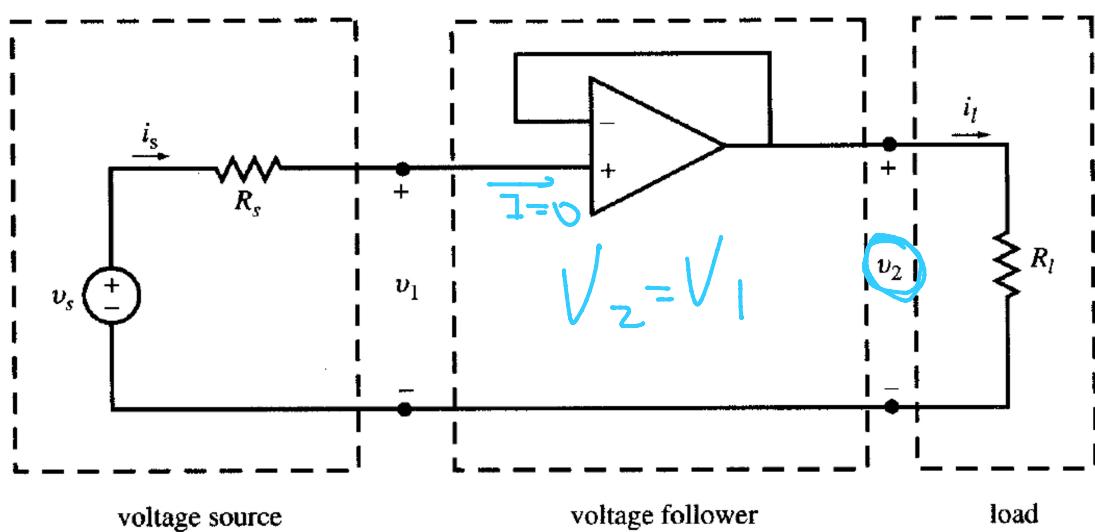


$$V_A$$

$$I_1 + I_2 + I_3 = 0 \Rightarrow$$

$$\frac{V_1 - V_A}{R} + \frac{V_2 - V_A}{R} + \frac{V_3 - V_A}{R} = 0 \Rightarrow$$

$$\Rightarrow 3V_A = V_1 + V_2 + V_3 \Rightarrow V_A = \frac{V_1 + V_2 + V_3}{3}$$




$$(3) V_A = -R_2 \cdot I$$

$$(1) V_A - V_B = R_1 \cdot I$$

$$\text{C } V_C - V_A = R_1 \cdot I \quad (2)$$

$$V_A - V_B = R_2 \cdot I \Rightarrow$$

$$V_B = V_A - R_2 \cdot I$$

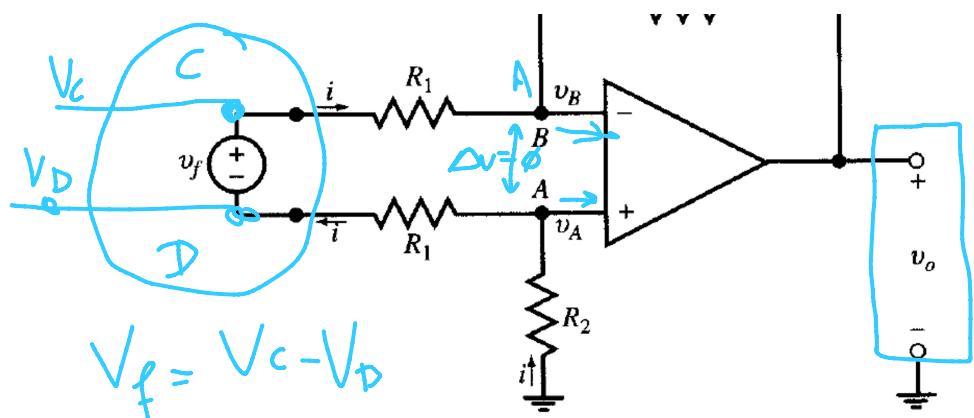


$$v_o = v_A \cdot k_2 + v_D$$

$$\Downarrow$$

$$v_o = -R_2 I - R_2 I$$

$$= -2R_2 I \quad \text{④}$$
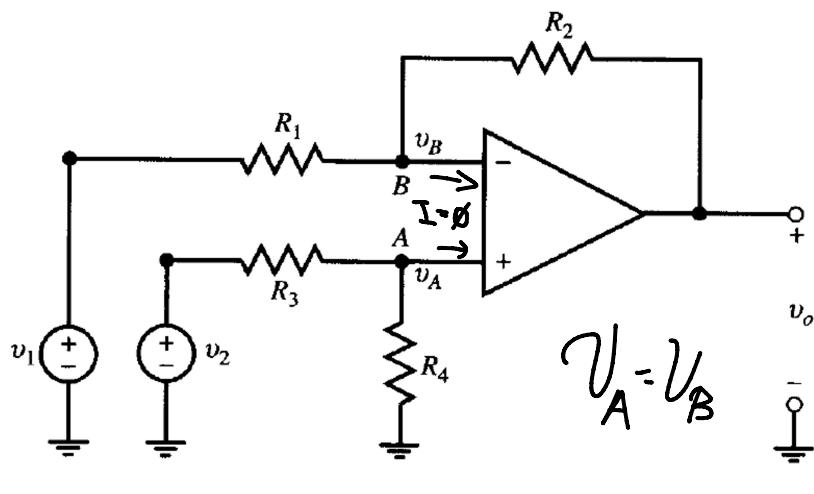
$$\begin{aligned} \textcircled{1} & \Rightarrow V_C - V_D = 2R_1 \cdot I \quad \textcircled{4} \\ \textcircled{2} & \Rightarrow V_C - V_D = -2R_1 \frac{V_o}{2R_2} \Rightarrow \\ & \Rightarrow V_o = -\frac{R_2}{R_1} (V_C - V_D) = \boxed{-\frac{R_2}{R_1} V_f = V_o} \\ & V_o = G V_f(t) \end{aligned}$$



$$\frac{v_A - v_2}{R_3} + \frac{v_A}{R_4} = 0$$

$$\frac{v_B - v_1}{R_1} + \frac{v_B - v_o}{R_2} = 0$$

$$R_3 = \cancel{4k\Omega}$$

$$R_1 = \cancel{1k\Omega}$$

$$R_2 = \cancel{2k\Omega}$$

$$v_o = \frac{R_4(R_1 + R_2)}{R_1(R_3 + R_4)} v_2 - \frac{R_2}{R_1} v_1$$

$$R_1 = R$$

$$R_2 = 2R_1$$

$$R_4 = R_3 + R_4 \Rightarrow R_2 = \cancel{4} - \Delta$$

$$\Rightarrow \frac{\cancel{4}R_4}{R(R_3 + R_4)} = \cancel{4}$$


$$R_4 = R_3 + R_4 \Rightarrow R_3 = v - R_4 \text{ at } t_1, t \in \mathbb{N}_P \Rightarrow \frac{1}{R(R_3 + R_4)} = \frac{1}{R}$$

ΠΥΚΝΩΤΗΣ - CAPACITOR


$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$\dot{i} = C \frac{dv}{dt}$$

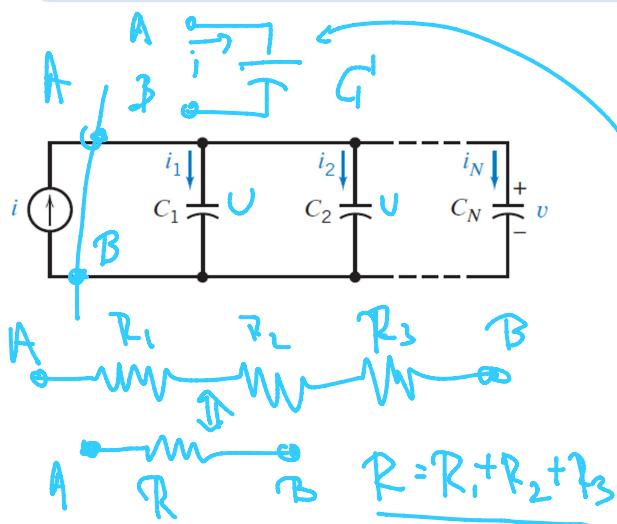The voltage across a capacitor cannot change instantaneously.


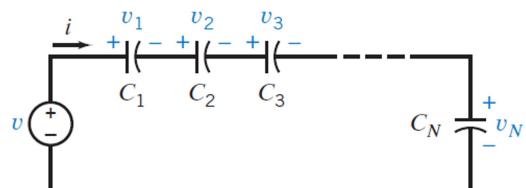
$$\begin{aligned} i &= i_1 + i_2 + i_3 + \dots + i_N \\ i &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt} \\ \dot{i} &= \left(\sum_{n=1}^N C_n \right) \frac{dv}{dt} \\ Y &= \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \end{aligned}$$



$$\begin{aligned} v &= v_1 + v_2 + v_3 + \dots + v_N \\ v &= \frac{1}{C_1} \int_{t_0}^t i d\tau + v_1(t_0) + \dots + \frac{1}{C_N} \int_{t_0}^t i d\tau + v_N(t_0) \\ &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i d\tau + \sum_{n=1}^N v_n(t_0) \\ &= \left(\sum_{n=1}^N \frac{1}{C_n} \right) \int_{t_0}^t i d\tau + \sum_{n=1}^N v_n(t_0) \end{aligned}$$

$$\frac{1}{C_s} = \sum_{n=1}^N \frac{1}{C_n}$$


ΕΜΑΓΓΗ - INDUCTOR

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

⇒ $V = L \frac{di}{dt}$



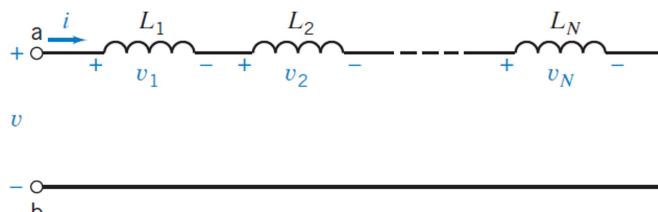
The current in an inductance cannot change instantaneously.



$$\begin{aligned} v &= v_1 + v_2 + \dots + v_N \\ &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\ &= \left(\sum_{n=1}^N L_n \right) \frac{di}{dt} \end{aligned}$$

$$L_s = \sum_{n=1}^N L_n$$

$$R = \sum_{i=1}^N R_i$$

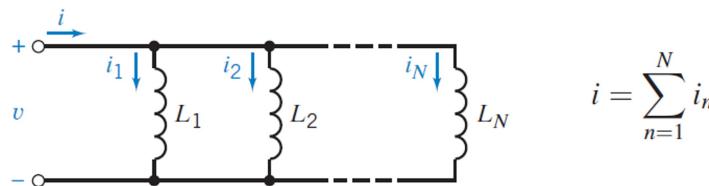

$$i = \sum_{n=1}^N i_n \quad i = \left(\sum_{n=1}^N \frac{1}{L_n} \right) \int_{t_0}^t v d\tau + \sum_{n=1}^N i_n(t_0)$$


$$\frac{1}{L_p} = \sum_{n=1}^N \frac{1}{L_n}$$

CAPACITOR

INDUCTOR

$$V = X_L \angle \phi$$


CAPACITOR

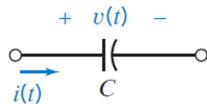

$$i(t) = C \frac{d}{dt} v(t)$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

INDUCTOR

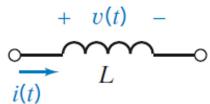


$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$v(t) = L \frac{d}{dt} i(t)$$





$$V = A \angle \varphi$$
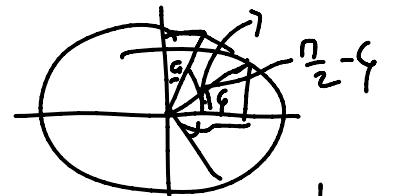
$$\begin{aligned} I_{H1} &= CA \sin(\omega t + \varphi) \cdot w \\ &= \underline{\omega C A} \cos\left(-\frac{P}{2} + \underline{\omega t + \varphi}\right) \end{aligned}$$







$$I(t) = \underline{\omega C A} \left[\varphi - \frac{\pi}{2} \right]$$

SERIES OR PARALLEL CIRCUIT

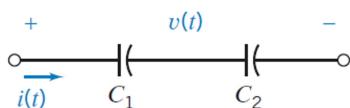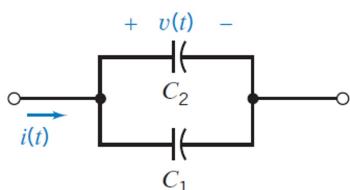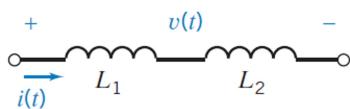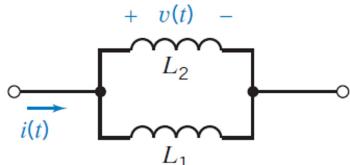

EQUIVALENT CIRCUIT

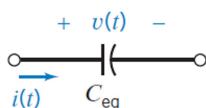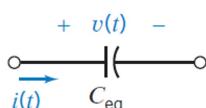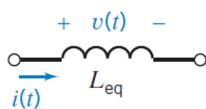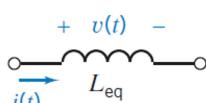

EQUATION



$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

$$L_{eq} = L_1 + L_2$$

$$C_{eq} = C_1 + C_2$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

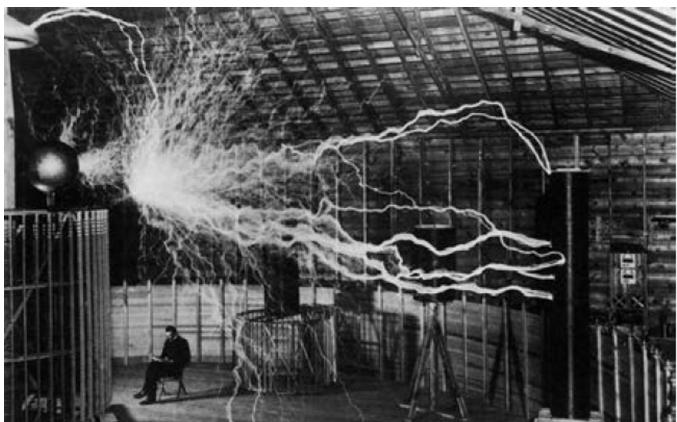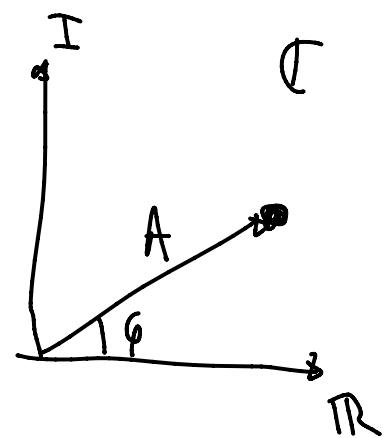
$$\frac{V}{I} = \underline{\omega C A} \left[\varphi - \frac{\pi}{2} \right] = Z$$



$$i_s = 100 \sin 400t \text{ A}$$

$$L = ? \text{ H}$$

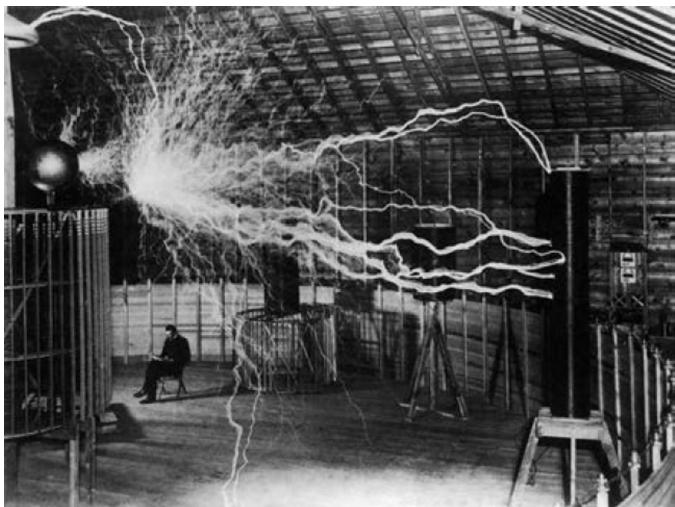
ΔΙΗΛΕΚΤΡΙΚΗ ΑΝΤΙΣΤΑΞΗ
ΑΓΡΑ: $3 \cdot 10^6 \frac{\text{V}}{\text{m}}$



$$i_s = 100 \sin 400t \text{ A}$$

$$L = ? \text{ H}$$

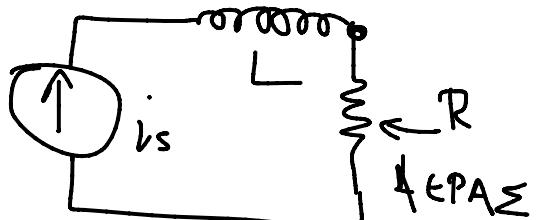
ΔΙΗΛΕΚΤΡΙΚΗ ΑΝΤΙΣΤΑΣΗ
ΑΕΠΑ: $3 \cdot 10^6 \frac{\text{V}}{\text{m}}$



$\sim 5 \text{ m}$

$$\frac{V_1}{500\text{V}} = \frac{100.000}{R} \quad \frac{V_2}{V_1} = \frac{m_2}{m_1}$$

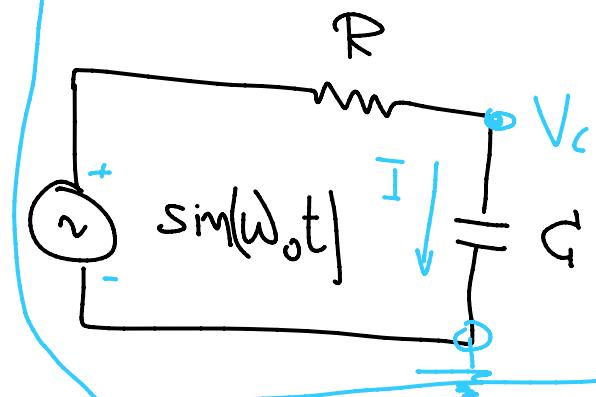
ΠΩΣΗ Η ΣΑΤΑΝΑΝΘΡΩΠΗ
ΕΝΕΡΓΕΙΑΣ ΕΤΩΝ ΠΥΚΝΩΤΗ;



$$i(t) = C \frac{d}{dt} v(t)$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$


$$\Phi = V \cdot I =$$

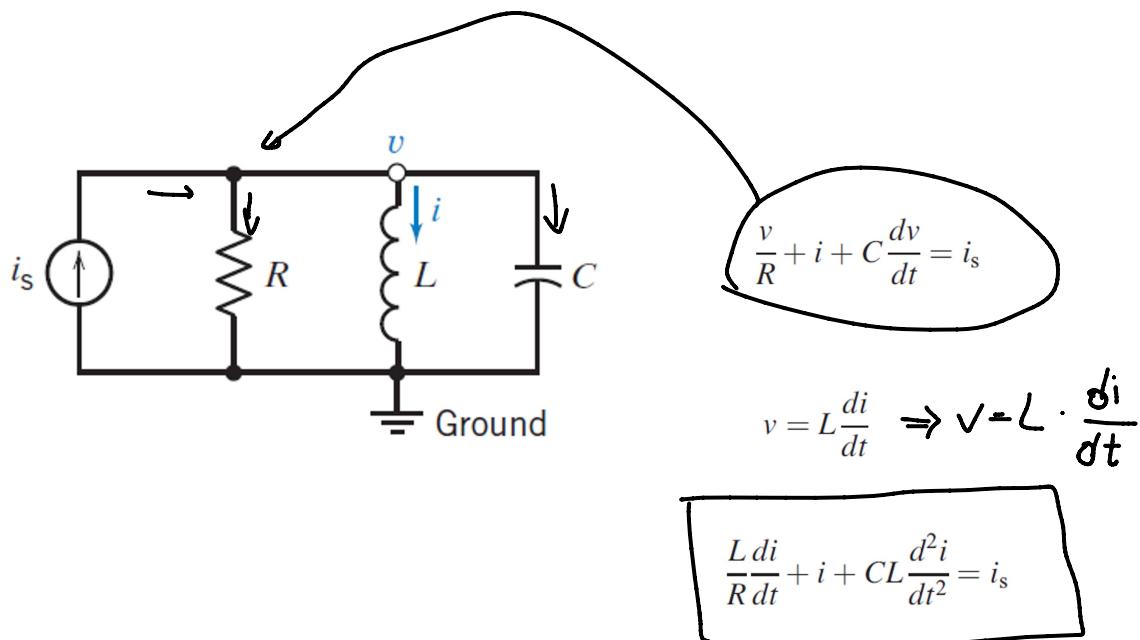

H. Hertz.

ΗΜΙΤΟΝΙΚΑ ΣΗΜΑΤΑ

$$\omega = 2\pi f = \frac{2\pi}{T}$$

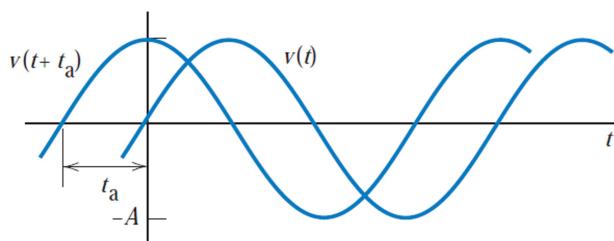

A phasor is a complex number that is used to represent the amplitude and phase angle of a sinusoid. The relationship between the sinusoid and the phasor is described by

$$A \cos(\omega t + \theta) \leftrightarrow A \angle \theta \quad (10.3-1)$$

Η ΙΑΤΟΣ *ΜΙΓΑ ΔΙΚΟΣ ΑΡΙΘΜΟΣ*
ΕΥΧΩΔΩΤΗ ΦΑΣΗ

\rightarrow EXPLAIN $\phi A \Sigma H$

The impedance of an element of an ac circuit is defined to be the ratio of the voltage phasor to the current phasor. The impedance is denoted as $Z(\omega)$ so


$$Z(\omega) = \frac{\mathbf{V}(\omega)}{\mathbf{I}(\omega)} = \frac{V_m \angle \theta}{I_m \angle \phi} = \frac{V_m}{I_m} \angle (\theta - \phi) \Omega \quad (10.4-2)$$

Diagram of a resistor: $A \cos(\omega t + \theta)$ $\stackrel{V}{\pm} = \frac{V_m \cos(\omega t + \theta)}{R} = R$

Arrangement: $Z_R(\omega) = \frac{V_m \cos(\omega t + \theta)}{I_m \angle \theta} = R$

XWPMZILCZM :
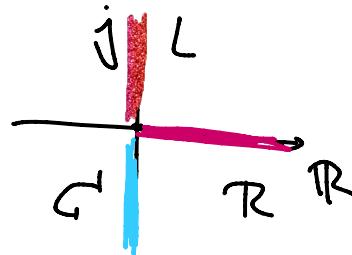
$$v_C(t) = A \cos(\omega t + \theta) \text{ V} \Rightarrow V_{\omega} = A \angle \theta$$




$$i_C(t) = C \frac{d}{dt} v_C(t) = -C \omega A \sin(\omega t + \theta) = C \omega A \cos(\omega t + \theta + 90^\circ) \text{ A}$$

$$\underline{V_C(\omega)} = A \angle \theta \text{ V} \text{ and } \underline{I_C(\omega)} = C \omega A \angle (\theta + 90^\circ) = (C \omega \angle 90^\circ)(A \angle \theta) = j \omega C A \angle \theta \text{ A}$$

$(\cancel{\omega \cos(\omega t + 90^\circ)} \cdot A \cos(\omega t + \theta))$

$$Z_C(\omega) = \frac{V_C(\omega)}{I_C(\omega)} = \frac{A \angle \theta}{j \omega C A \angle \theta} = \frac{1}{j \omega C} \Omega$$
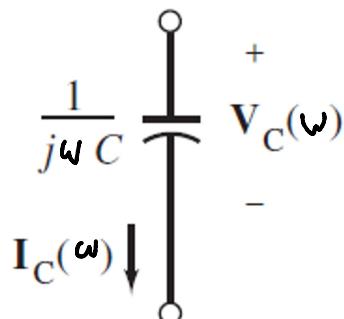
$$Z_C(\omega) = - \cdot \frac{j}{\omega C}$$




ΕΠΑΓΓΕΛΜΑΤΙΚΗ


$$v_L(t) = L \frac{d}{dt} i_L(t) = -L\omega A \sin(\omega t + \theta) = \underline{L\omega A \cos(\omega t + \theta + 90^\circ)} \text{ V}$$

$$\underline{\mathbf{I}_L(\omega) = A \angle \theta \text{ A}} \text{ and } \mathbf{V}_L(\omega) = L\omega A \angle (\theta + 90^\circ) = j\omega LA \angle \theta \text{ V}$$
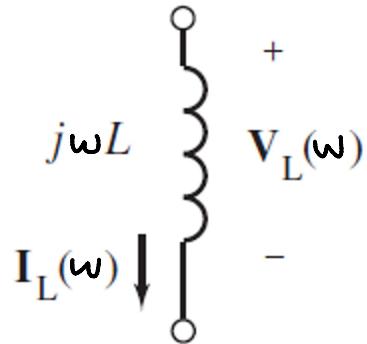
$$\mathbf{Z}_L(\omega) = \frac{\mathbf{V}_L(\omega)}{\mathbf{I}_L(\omega)} = \frac{j\omega LA \angle \theta}{A \angle \theta} = \underline{j\omega L \Omega}$$



A 6 KM Gm:

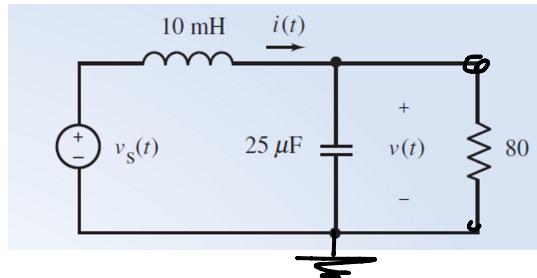


$$v_s(t) = 48 \cos(500t + 75^\circ) \text{ V}$$

Υπολογισε το $V(t)$

$$\mathbf{Z}_C(\omega) = \frac{1}{j\omega C} = \frac{1}{j500(25 \times 10^{-6})} = \frac{80}{j} = \underline{-j80 \Omega},$$

$$\mathbf{Z}_L(\omega) = j\omega L = j500(0.1) = j50 \Omega$$

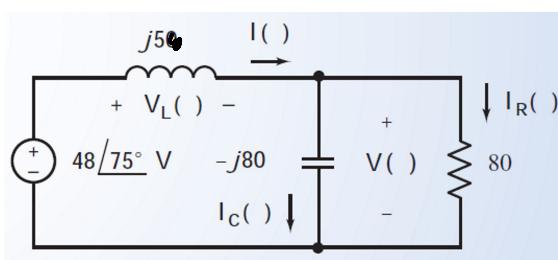
$$\mathbf{Z}_{CR} = \frac{80(-j80)}{80 - j80} = \frac{-j80}{1 - j} = \frac{80}{1 + j}$$




$$\mathbf{V}_L(\omega) = j50 \mathbf{I}(\omega), \quad \mathbf{I}_C(\omega) = \frac{\mathbf{V}(\omega)}{-j80} \text{ and } \mathbf{I}_R(\omega) = \frac{\mathbf{V}(\omega)}{80}$$


$$\mathbf{I}(\omega) = \mathbf{I}_C(\omega) + \mathbf{I}_R(\omega) = \frac{\mathbf{V}(\omega)}{-j80} + \frac{\mathbf{V}(\omega)}{80}$$
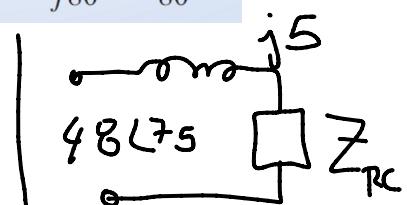
$$48 \angle 75^\circ = \mathbf{V}_L(\omega) + \mathbf{V}(\omega) = j50 \mathbf{I}(\omega) + \mathbf{V}(\omega)$$



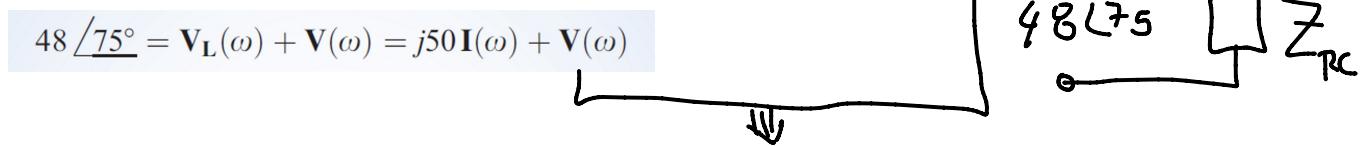
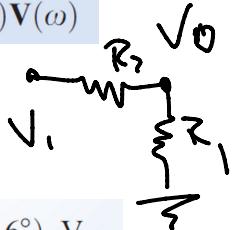
$$48 \angle 75^\circ = j50 \left[\frac{\mathbf{V}(\omega)}{-j80} + \frac{\mathbf{V}(\omega)}{80} \right] + \mathbf{V}(\omega) = \left[\frac{j50}{-j80} + \frac{j50}{80} + 1 \right] \mathbf{V}(\omega) = [-0.625 + j0.625 + 1] \mathbf{V}(\omega) = (0.375 + j0.625) \mathbf{V}(\omega)$$



$$\mathbf{V}(\omega) = \frac{48 \angle 75^\circ}{0.375 + j0.625} = \frac{48 \angle 75^\circ}{0.7289 \angle 59^\circ} = 65.9 \angle 16^\circ \text{ V} \quad \Rightarrow \quad v(t) = 65.9 \cos(500t + 16^\circ) \text{ V}$$

$$\frac{V(\omega)}{48 \angle 75^\circ} = \frac{\frac{80}{1+j}}{\frac{80}{1+j} + \frac{5j(1+j)}{1+j}} \Rightarrow V(\omega) = 48 \angle 75^\circ$$

$Z_R = R \quad Z_C = \frac{1}{j\omega C} \quad Z_L = j\omega L$

ΤΑΟΗΤΙΚΑ ΦΙΝΤΡΑ ΜΕ ΕΛΣΟΠΕΣ

Diagram of a series RLC circuit with input voltage V_i and output voltage V_o .



$$\left| \frac{V_o}{V_i} \right| = \left| \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right| = \left| \frac{1}{1 + j\omega RC} \right| = \left| \frac{V_o}{V_i} \right| \quad (\text{dB})$$

$$= |1 + j\omega RC|^{-1} \quad \omega = 2\pi f$$


$$= \left| 1 + j\omega RC \right|^{-1}$$




$$f = \frac{1}{2\pi RC}$$

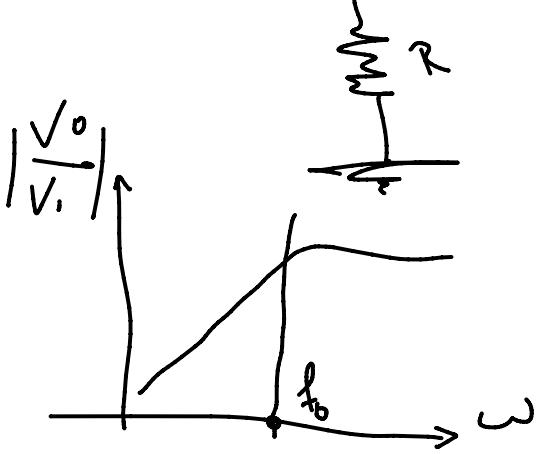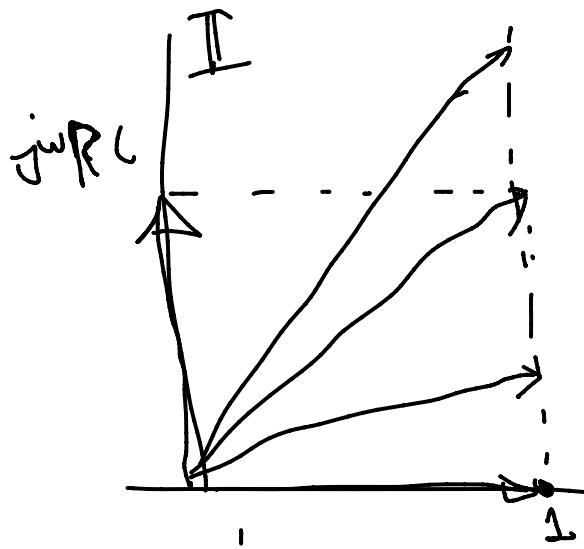

$$\begin{aligned} \left| \frac{V_o}{V_i} \right| &= \left| \frac{R}{R + \frac{1}{j\omega C}} \right| = \\ &= \left| \frac{1}{1 + \frac{1}{j\omega RC}} \right| \quad f_o = \frac{1}{2\pi R C} \end{aligned}$$

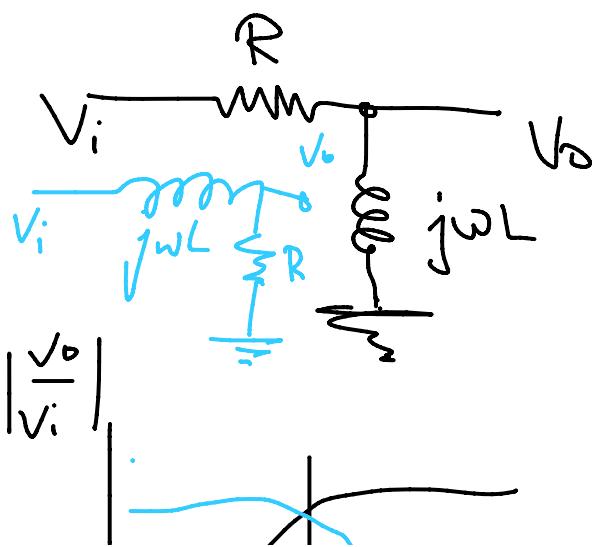


$$\begin{aligned} \left| \frac{V_o}{V_i} \right| &= \left| \frac{j\omega L}{R + j\omega L} \right| = \\ &= \left| \frac{1}{1 + \frac{R}{j\omega L}} \right| = \end{aligned}$$

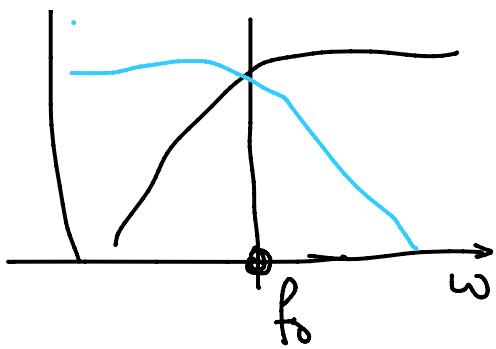

$$= \left| 1 + \frac{R}{j\omega L} \right|^{-1}$$

$$f_0 = \frac{R}{2\pi\omega L}$$

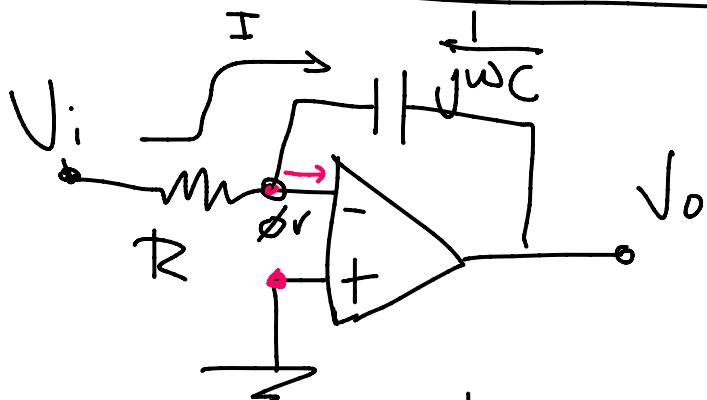

ENERGIA

$$\left| \frac{V_o}{V_i} \right| = \left| \frac{-\frac{1}{j\omega C}}{\frac{1}{R} - \frac{1}{j\omega C}} \right| = \left| \frac{\frac{1}{j\omega RC}}{\frac{1}{j\omega RC}} \right| = \frac{1}{\omega RC}$$




$$20 \log_{10} \left| \frac{V_o}{V_i} \right| =$$

$$= 20 \log \frac{1}{\omega RC} =$$

$$\omega \rightarrow \infty \Rightarrow G = -\frac{R}{\omega L}$$
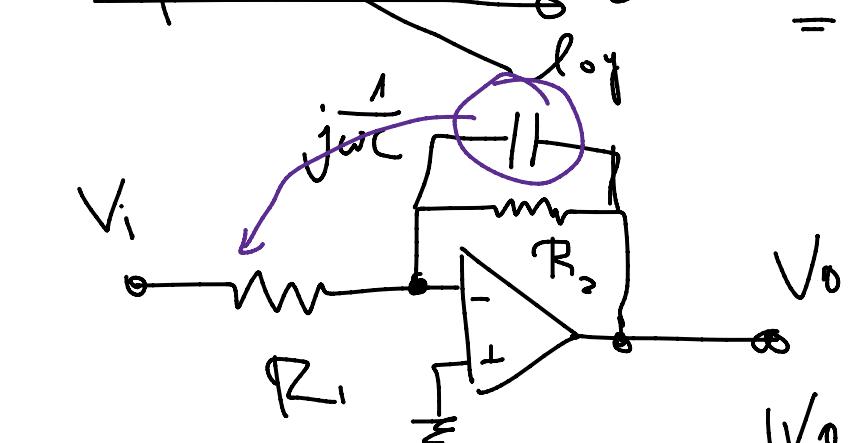
$$\omega \rightarrow 0 \Rightarrow G = \phi$$





$$\left| \frac{V_o}{V_i} \right| \xrightarrow{B \neq \phi}$$

$$= \frac{R_2 \cdot \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_i} = - \frac{\frac{R_2 \cdot j\omega C}{R_2 + j\omega C}}{R_1} =$$

$$\Rightarrow \left| \frac{V_o}{V_i} \right| = \frac{\left| R_2 \frac{1}{j\omega C} \right|}{\left| R_1 R_2 + \frac{R_1}{j\omega C} \right|} = \frac{\frac{R_2}{\omega C}}{\left| R_1 R_2 + \frac{R_1}{j\omega C} \right|} =$$


$$= \frac{R_2}{R_1 \left| \omega C R_2 + \frac{j}{j} \right|} = \frac{R_2}{R_1 \left| \omega C R_2 - j \right|}$$

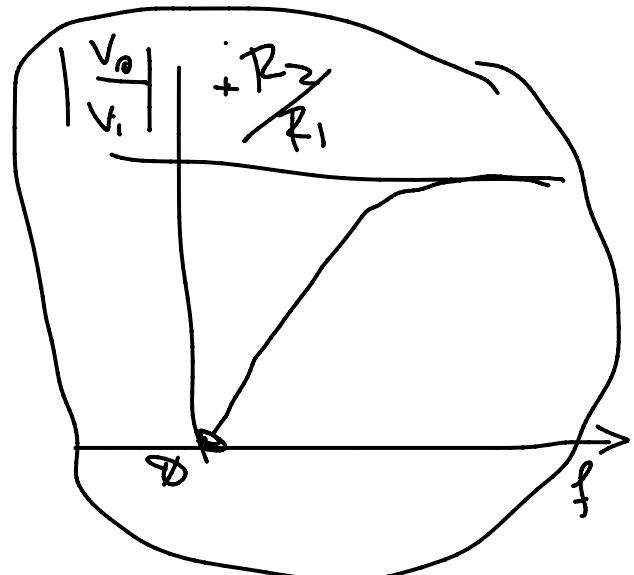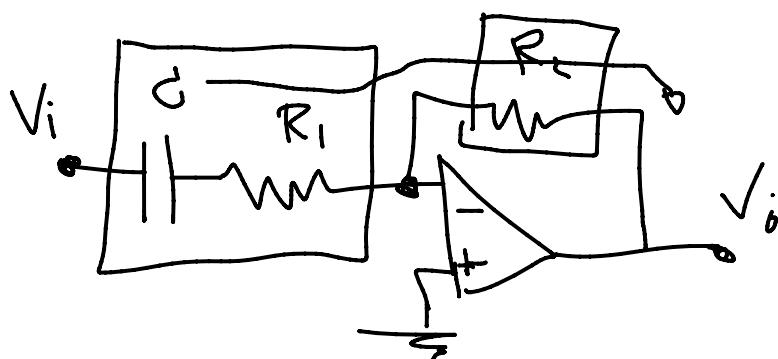

$$\left| \frac{V_o}{V_i} \right| = \left| - \frac{R_2}{R_1 + \frac{1}{j\omega C}} \right| =$$

$$= \left| \frac{R_2}{R_1 + \frac{1}{j\omega C}} \right|$$



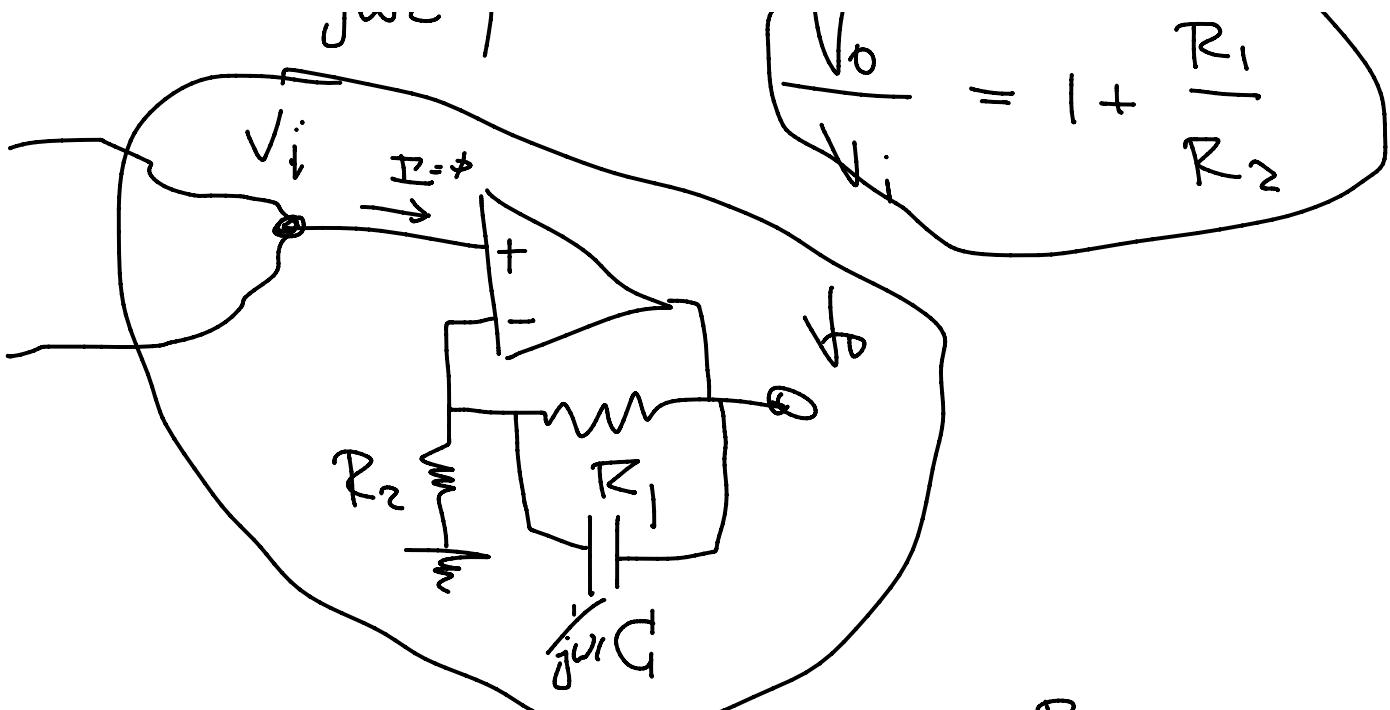
$$\frac{V_o}{V_i} = 1 + \frac{R_1}{R_2}$$



$$\frac{V_o}{V_i} = 1 + \frac{\frac{R_1 \cdot \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}}}{R_2} = 1 + \frac{\frac{R_1}{1 + j\omega R_1 C}}{R_2}$$

$$= 1 + \frac{\frac{R_1}{R_2 + j\omega R_1 R_2 C}}{1 + j\omega R_1} = 1 + \frac{\frac{R_1}{R_2}}{1 + j\omega R_1} - \frac{1}{1 + j\omega R_1}$$

$$\left| \frac{V_o}{V_i} \right| = \left| 1 + \frac{R_1}{R_2} \cdot \frac{1}{1 + j\omega R_1} \right|$$

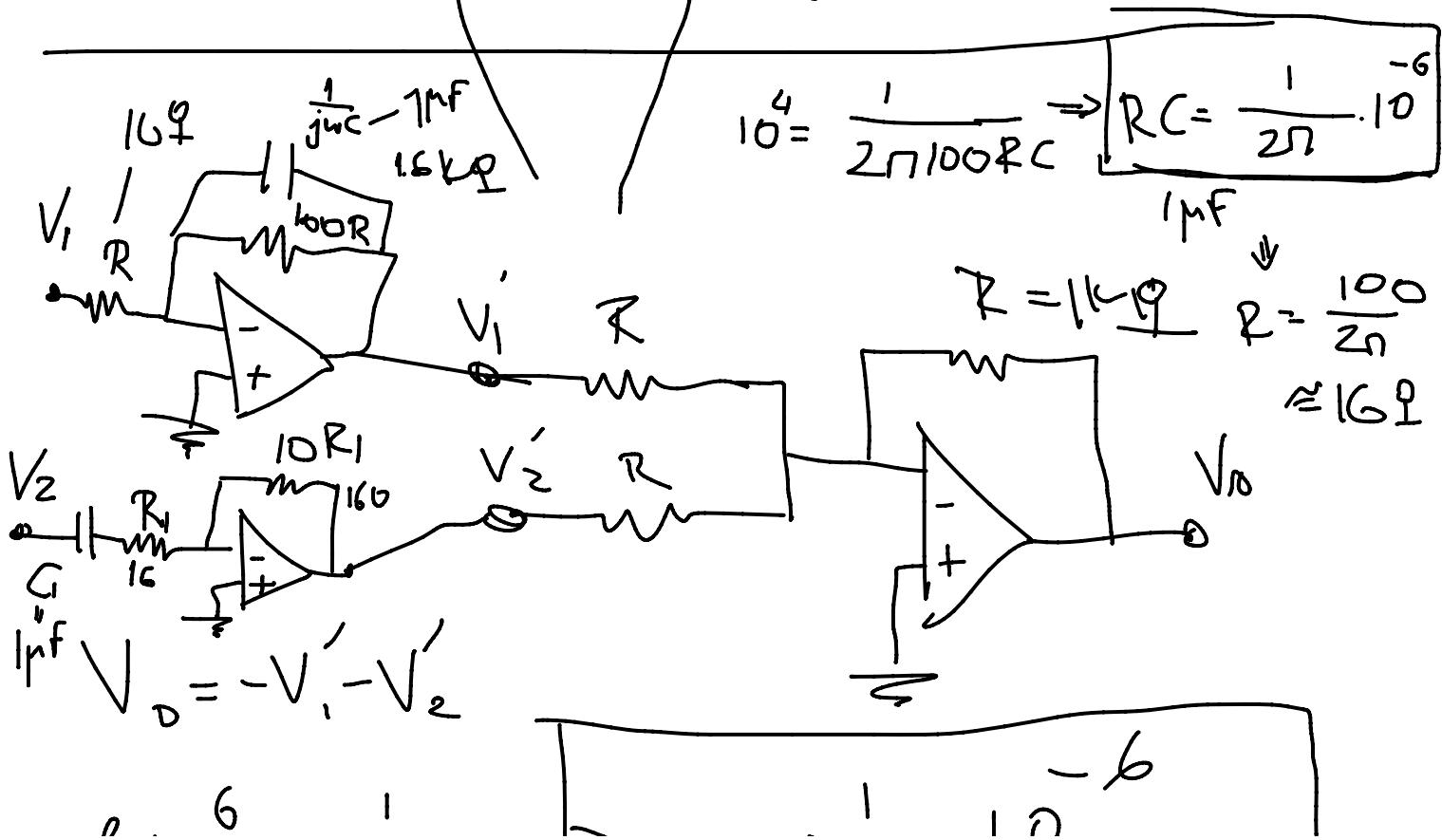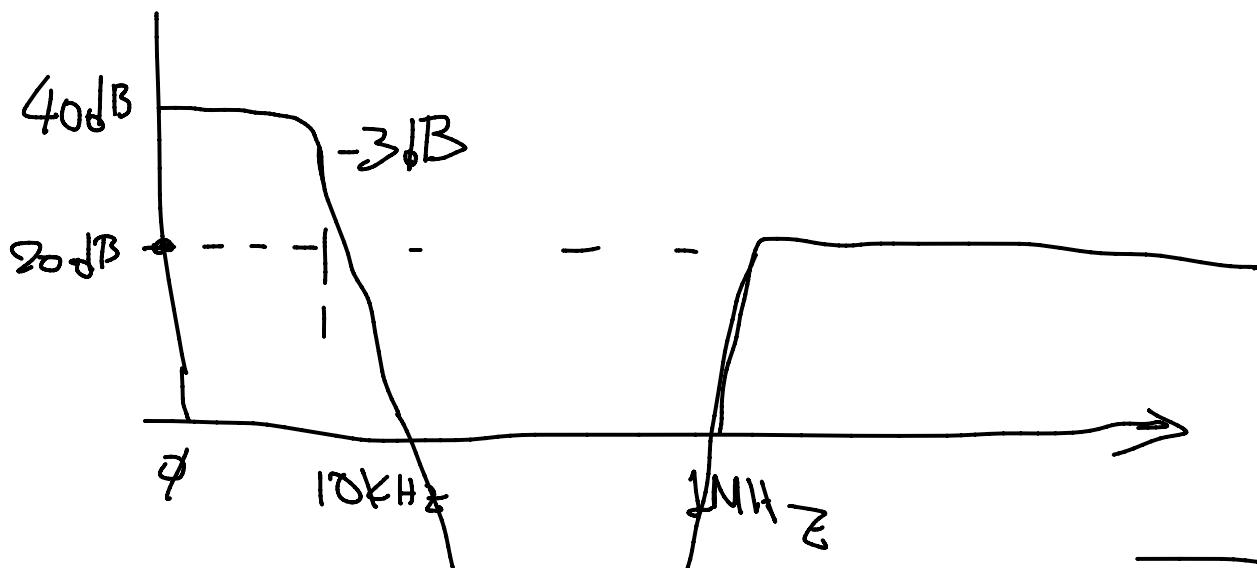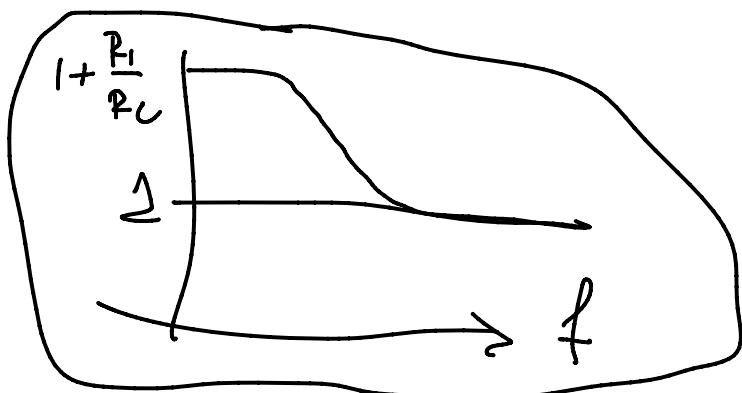


$$f = 10^6 = \frac{1}{2\pi R_1 C_1} \Rightarrow R_1 C_1 = \frac{1}{2\pi} \cdot 10^{-6}$$

$$\frac{10 R_1}{R_1 + \frac{1}{j\omega C}} = 10 \frac{1}{1 + \frac{1}{j\omega R_F}}$$

$$f = \frac{1}{2\pi R_C} = \frac{1}{2\pi \cdot 10^{-6} \cdot R} = 10^6 \Rightarrow$$

$$R = \frac{1}{2\pi} 10^{-2} = 1.6 \cdot 10^{-2}$$

$$G = \text{Im } F$$

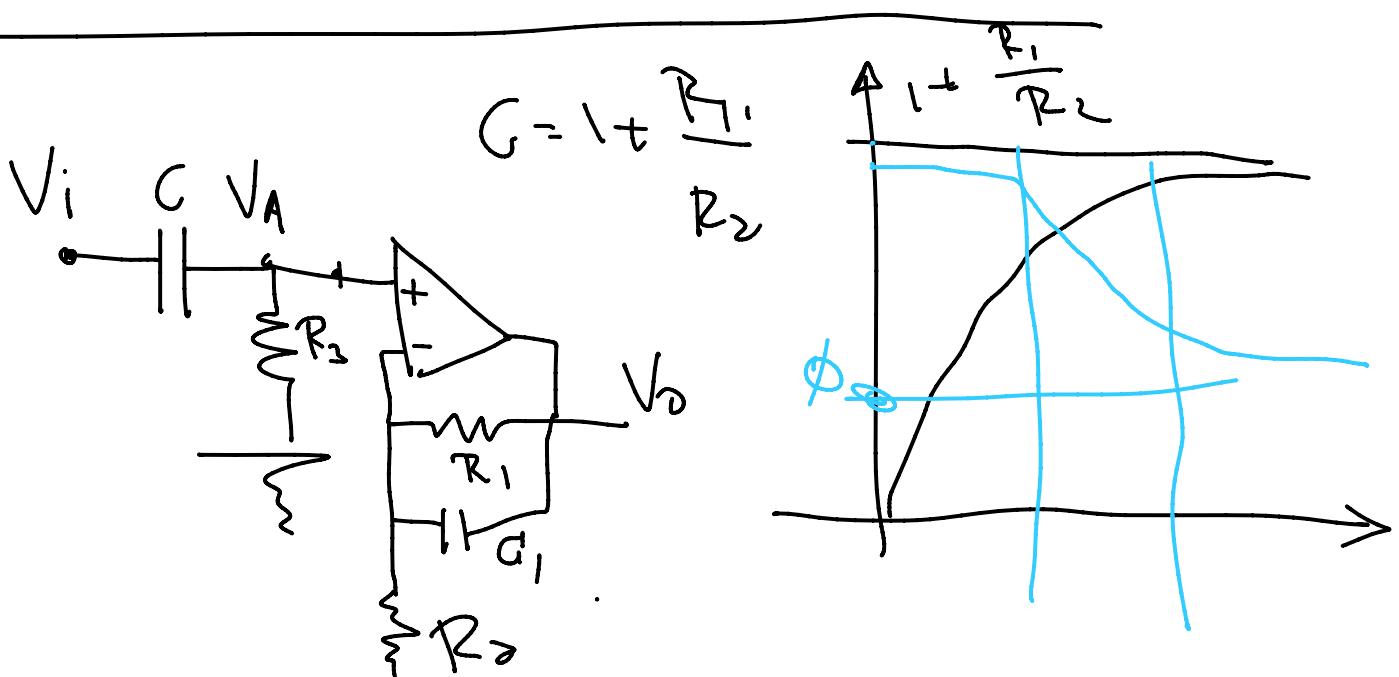

$$\left| \frac{V_o}{V_i} \right| = \left| \left(1 + \frac{\frac{R_1}{j\omega C_1}}{R_0 + \frac{R_1}{j\omega C_1}} \right) \cdot \frac{R_3}{R_3 + \frac{1}{j\omega C}} \right| = \left| \frac{V_o}{V_{in}} \right| \cdot \left| \frac{V_A}{V_i} \right|$$

EN.K. ↓ NAD.

$$\frac{1}{2\pi R_C} = 0.15 \cdot 10^{-3} \cdot 10^{+9} = 15 \text{ kHz}$$

