
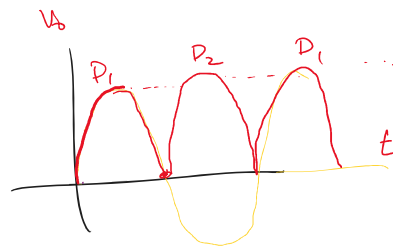



$$I = I_s \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$n = 1.2$$

$$V_T = 25 \text{ mV}$$

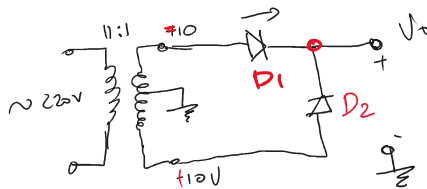


ZENER.

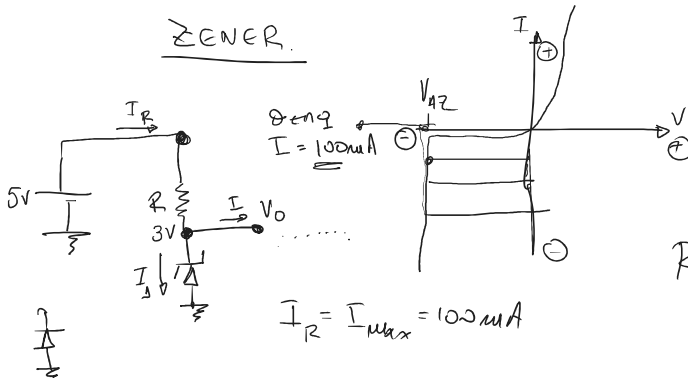

$$V_{Z2} = 3V$$

$$R = \frac{5V - 3V}{100 \mu A} = \frac{2V}{0.1A}$$

$$R = 20 \Omega$$

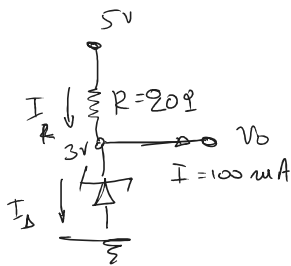


$$I_R = \frac{5V - 3V}{20} = \frac{2}{20} = 100 \mu A$$

$$I = 100 \mu A$$

$$I_R = I_D + I \Rightarrow I_D = \phi$$


$$P_W = 5V \times 0.1A = 0.5W$$

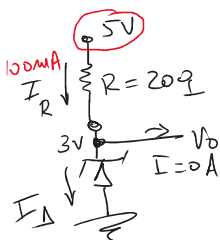

$$I_R = \frac{5V - 3V}{20 \Omega} = 100 \mu A$$

$$I_R = I_D + I \Rightarrow I_D = 100 \mu A$$

$$P_{ZENER} = 3V \times 0.1A = 0.3W$$

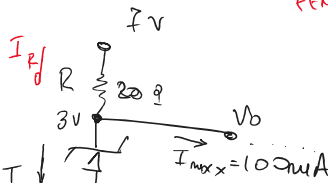



$$I_R = \frac{7V - 3V}{20 \Omega} = \frac{4}{20} = 200 \mu A$$

$I_{min} = 0 \text{ mA}$

$I_{Zmin} = I_P - I_{max} = 200 \text{ mA} - 100 \text{ mA} = 100 \text{ mA}$

$I_{Zmax} = I_P - I_{min} = 200 \text{ mA} - 0 = 200 \text{ mA}$

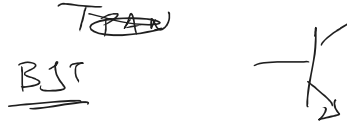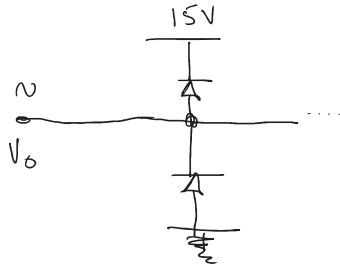$\alpha\eta\theta\Delta\theta\epsilon\eta = \frac{P_{\lambda\eta\theta\epsilon}}{P_{\epsilon\eta}} = \frac{3\text{V} \times 0.1\text{A}}{7\text{V} \times 0.2\text{A}} = \frac{3}{14} \times 100\%$



- ΔΙΟΔΟΙ
- LED
- Φθ τσΔΙΟΔΟΙ
- ΖΕΝΕΡ.