

ANALOGICA

Jan. 14

7250 → 3	• 6296 → 5	• 7361 → 3	6376 → ∅
• 7237 → 3	• 7362 → 5	• 7867 → 5	6881 → 2
7296 → 3	6734 → 5	7442 → 5	7886 → 2
7724 → 5	• 7784 → 5	• 7192 → 5 ?	• 7792 → 5
6473 → 2	6953 → 3	• 7239 → 5	7895 → 5
7071 → 2	• 7738 → 5	7410 → 3	6639 → 5
7966 → 2	7841 → 4	7459 → 2	
7838 → 5	• 7056 → 3	• 7268 → 5	
7483 → 2	? 7005 → 3	7129 → 2	
6754 → 3	7877 → 3	• 7494 → 3	
• 7737 → 3	• 7388 → 5	7606 → 3	
5608 → 2	7055 → 5	• 7931 → 5	
7063 → 5	• 7290 → 5	• 7281 → 5	
7910 → 5	• 7130 → 3	• 7225 → 5	
• 7811 → 3	6332 → 5	7716 → 7	
7157 → 2	7184 → 2	• 7438 → 3	
• 7953 → 5	7042 → 3	7015 → 5	
7572 → 2	7365 → 3	7882 → 4 ?	
7144 → 2	6998 → 2	7840 → 4 ?	
• 7093 → 3	7926 → 5	• 6926 → 5	
7913 → 2	7107 → 2	5128 → 5	
6978 → 3	6 6363 → 5,5	7821 → 3	
7405 → 3	7826 → 3	7662 → ∅	
• 7347 → 5	7283 → 3	7796 → ∅	
7186 → 5	• 7733 → 5	6888 → 3	
• 7040 → 5	• 7218 → 5	7306 → 3	
• 7387 → 3	6915 → 3	7758 → 0	
• 7049 → 5	• 7351 → 5	7509 → 3	

① Για $V_1 = V_2 = 0$ πρέπει $V_0 \approx 0$
 $V_{C1} = V_{C2} \approx V_{CC} - \frac{I_1 R_c}{2}$ $V_{CE1} = V_{CE2} = V_{CC} - \frac{I_1 R_c}{2} + V_{BE}$
 Για να τρέχει σωστά R_c : $V_{BE3} \approx 0.7V \Rightarrow I_{C3} = \frac{V_{EE}}{R_c}$, $V_{CE3} = V_{CC}$
 $V_{BE3} = V_T \ln \left(1 + \frac{I_{C3}}{I_{S3}} \right) \iff I_{S3} = 1.07 \times 10^{-15} A$
 $Q_1: (74.3 \mu A, 14.4V)$ $Q_2: (74.3, 15V)$ $Q_3: (750 \mu A, 15V)$

② α) $A_H(s) = \frac{(1 + \frac{s}{2 \times 10^5}) \times 10^2}{(1 + \frac{s}{10^5}) (1 + \frac{s}{5 \times 10^5})}$ $f_{p1} = -10^5 \text{ rad/sec}$ $f_{z1} = -2 \times 10^5 \text{ rad/sec}$
 $f_{p2} = -5 \times 10^5 \text{ rad/sec}$
 $A_{MB} = 40 \text{ dB}$, $f_{3dB} = 21.7 \text{ kHz}$

β) $\omega_{p1} = \frac{1}{(R_c || R_i) (C_{GD} + \frac{C_{GS}}{1 + g_m R_c})}$ $A_{MB} = 0.705$
 $\omega_{p2} = \frac{1}{(\frac{1}{g_m} || R_L) (C_{GS} + C_L)}$ $f_{3dB} = 51.0 \text{ MHz}$

③ cascode CE-CB: $\omega_{p1} = \frac{1}{(r_{\pi1} || R_i) (C_{\pi1} + C_{\mu1} (1 + \frac{g_{m1}}{g_{m2}}))} \approx \frac{1}{r_{\pi1} || R_i (C_{\pi1} + 2C_{\mu1})}$
 $\omega_{p2} = \frac{1}{R_L (C_{\mu2} + C_L)}$ $A_{MB} = \frac{R_{T1}}{r_{\pi1} r_{\pi2}} \cdot g_{m1} \cdot \frac{1}{g_{m2}} = \frac{R_L}{r_{\pi2}} \cdot \frac{g_{m1}}{g_{m2}}$
 $A_{MB} = -152.8$, $\omega_{p1} = 11.6 \text{ MHz}$ & $\omega_{p2} = 7.02 \text{ MHz}$

④ $V_{B1} = 0$ $V_{E1} = -0.7V \Rightarrow I_{E1} = \frac{-0.7V - (-10)V}{4.3K} = 1 \text{ mA}$ $V_{C1} = 10 - I_1 R_3 = 9V$
 $I_{E2} = \frac{10V - (9 - V_{BE2})}{R_4} = 1 \text{ mA}$ $V_{C2} = -0.7V$
 $\Rightarrow I_{R2} = 0 = \frac{V_{C2} - V_{E1}}{R_2}$ $\phi_{\omega_{p1}} = \phi_{\omega_{p2}} = 40(0.001) = 0.045$
 $r_{\pi} = \frac{100}{g_m} = 2500 \Omega$, $r_o = \infty$ $A_v = 6.68$

Για το R_i τι $\approx 31.7 \text{ k}\Omega$
 $R_{out} = 2.11 \text{ k}\Omega$. A_v ≈ 6.68
 Το $A_v = 15$ $R_i = 100$. $R_o = 100$ $A_v = 6.68$, $R_{in} = 96 \text{ k}\Omega$, $R_{out} = 610 \Omega$