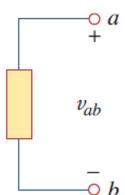


Voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).



$$v_{ab} \triangleq \frac{dw}{dq}$$

where w is energy in joules (J) and q is charge in coulombs (C).

$$\begin{aligned} P_{AN} &= 12 \cdot (+12) = 144 \text{ W} \\ P_{MP} &= 12 \cdot (-12) = -144 \text{ W} \end{aligned}$$

$$V \cdot I = \frac{dw}{dq} = \frac{dw}{dq} \cdot \frac{dq}{dt} = P$$

12A


$$V \quad I$$

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$

$p = vi$

$\sum p = 0$


Αρχή διατήρησης ενέργειας

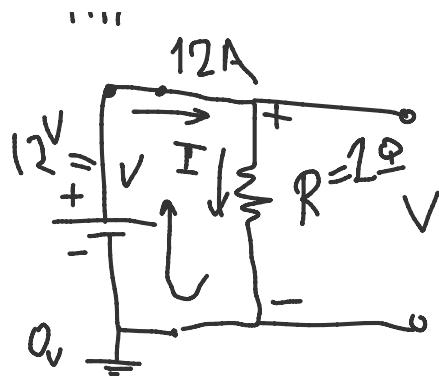




$$R = \frac{V}{I}$$


$$I = \frac{V}{R} = \frac{12}{1} = 12A$$

Ηλεκτρικά Στοιχεία


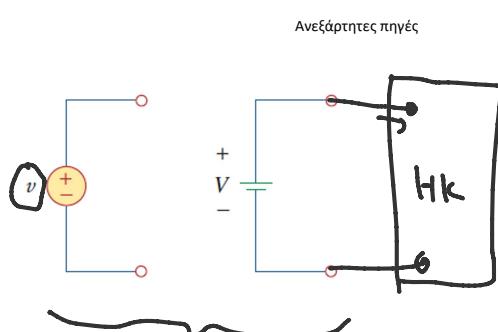


Εξαρτημένες πηγές

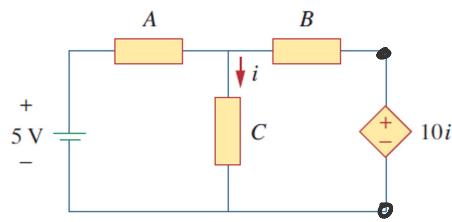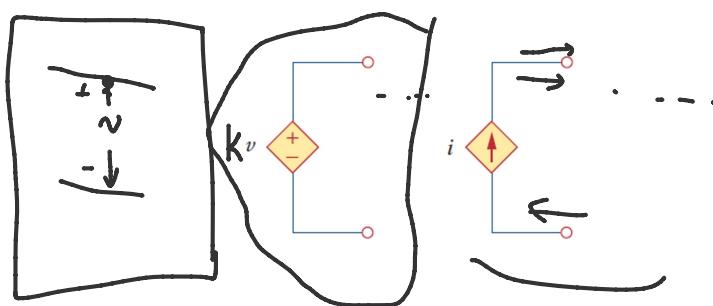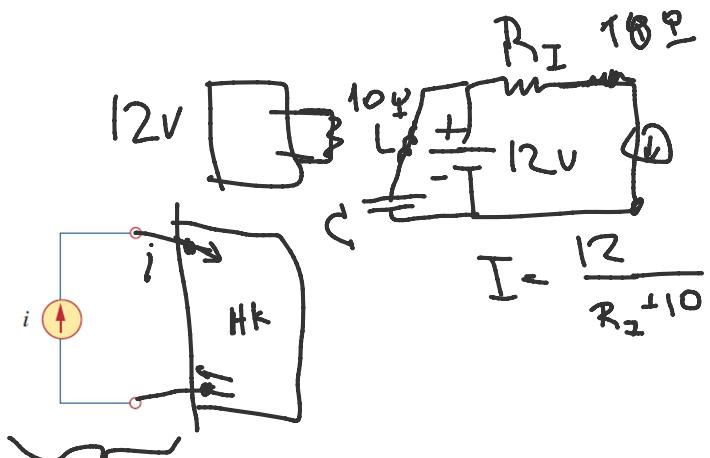

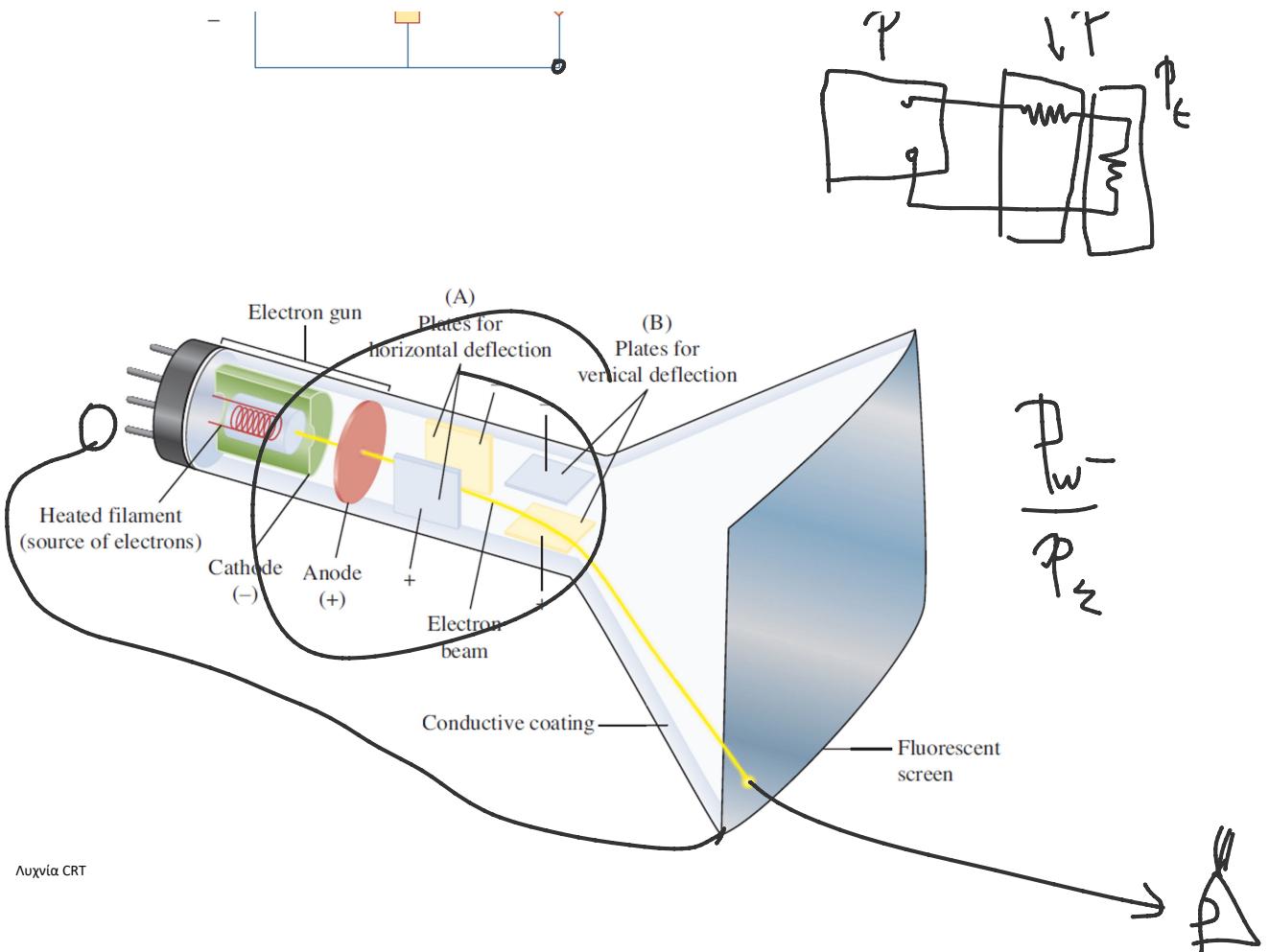



Αντίσταση

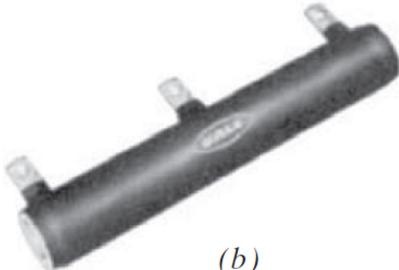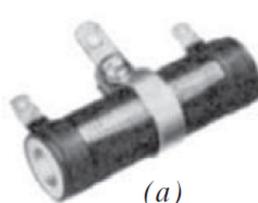

Courtesy of Vishay Intertechnology, Inc.

$$V = \sqrt{P \cdot R} = \sqrt{\frac{1}{4} \cdot 1} = 0.5V$$

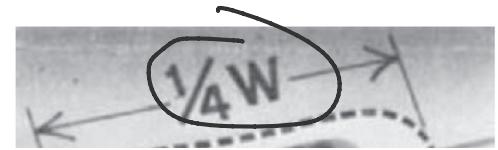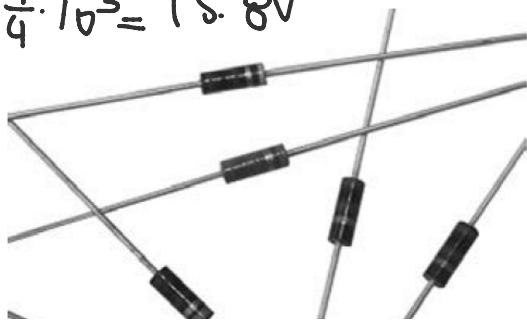
$$V = \sqrt{\frac{1}{4} \cdot 10^3} = 15.8V$$



$$R = 1\Omega \quad R = 1k\Omega$$


$$P = V \cdot I = R I^2 = \frac{V^2}{R}$$
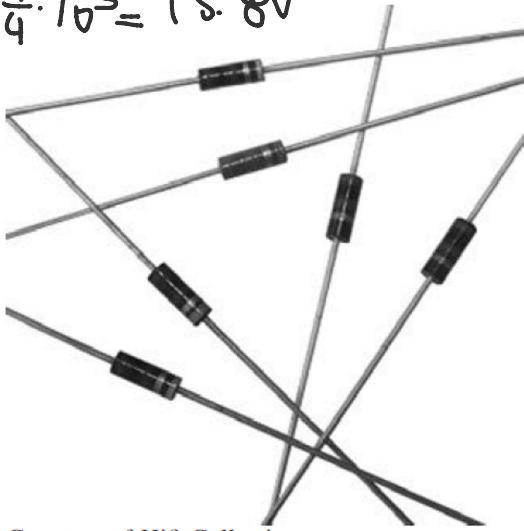
$$V = \sqrt{\frac{1}{4} \cdot 10^3} = 15.8V$$




Courtesy of Hifi Collective.
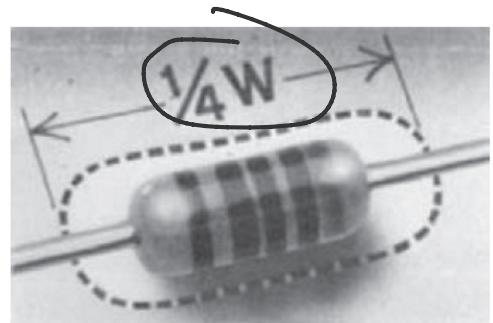
$$P = V \cdot I = R I^2 = \frac{V^2}{R}$$














Courtesy of Vishay Intertechnology, Inc.

FIGURE 2.4-7 A 1/4-watt metal film resistor. The body

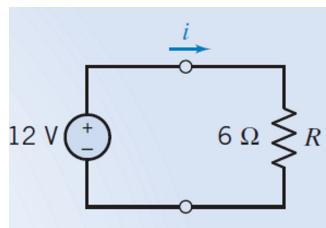

$$V = RI$$

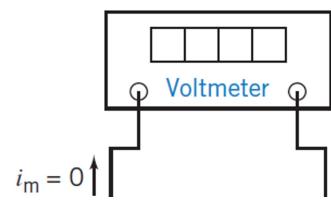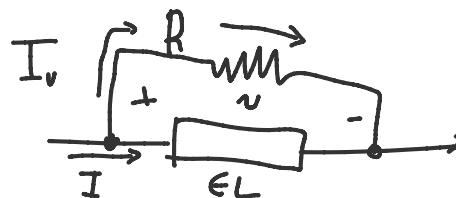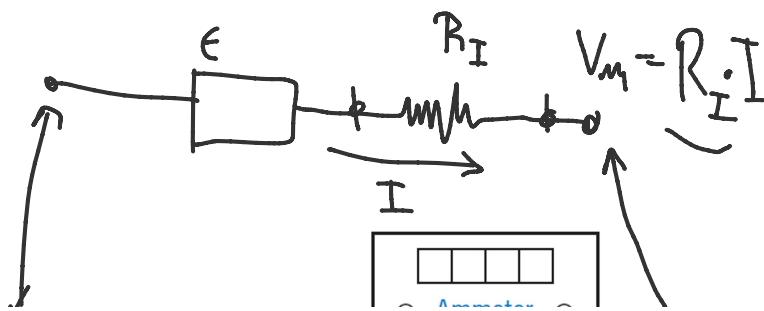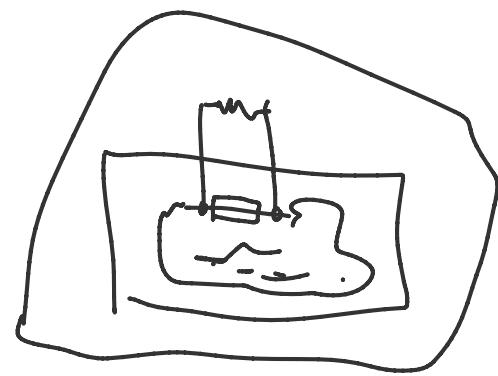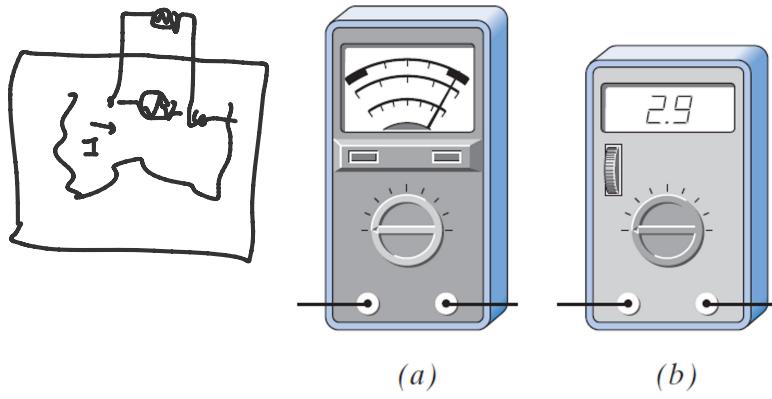

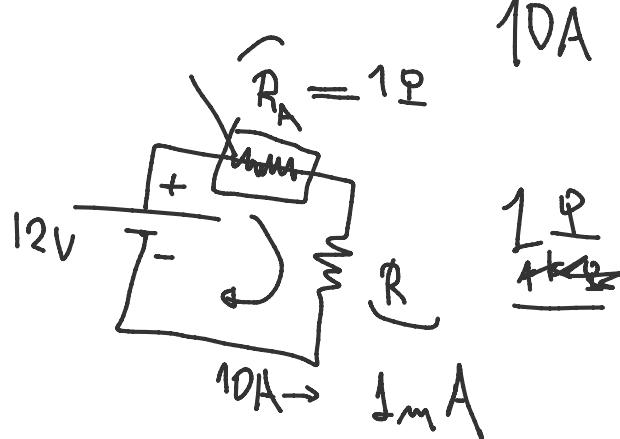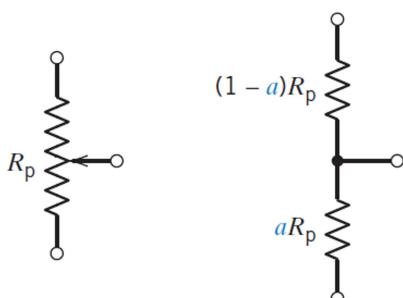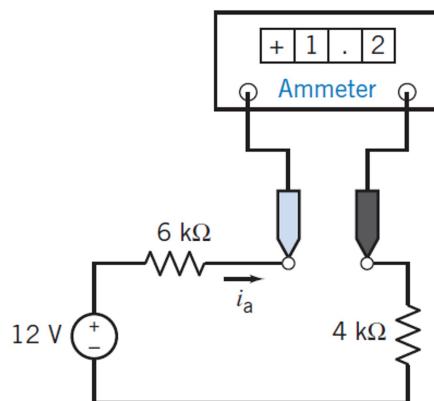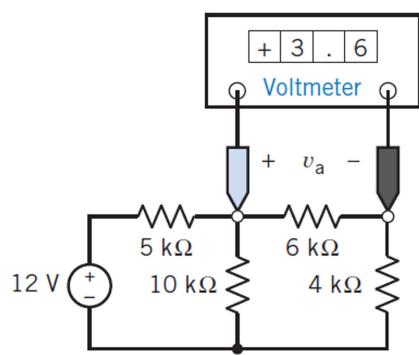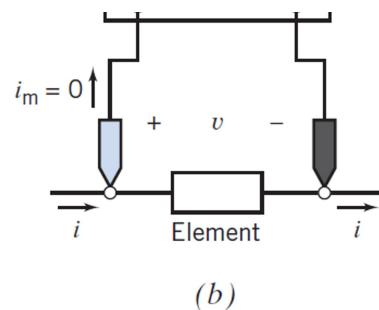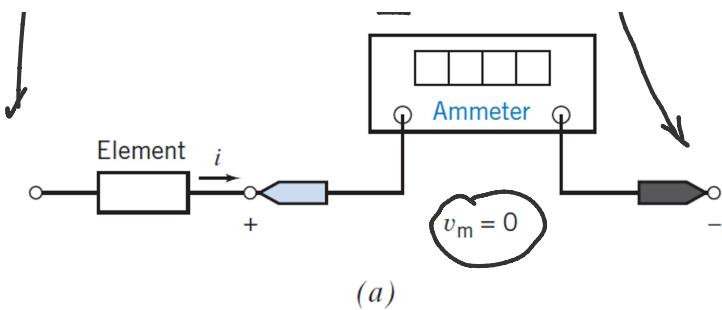

$$I = I_m A$$

Ποντεσόμετρα

$$R = \frac{12V}{10^{-3}A} = 12\text{ k}\Omega$$


$$1\Omega = (R+1) \cdot 10^{-3} \Rightarrow R = 12000 - 1 \approx 12\text{ k}\Omega$$


$$R = \frac{V}{I} = \frac{12}{10} = 1.2\text{ }\Omega$$

$$12V = (R+1) \cdot 10 \Rightarrow$$

$$12V = R \cdot 10 + 10 \Rightarrow$$
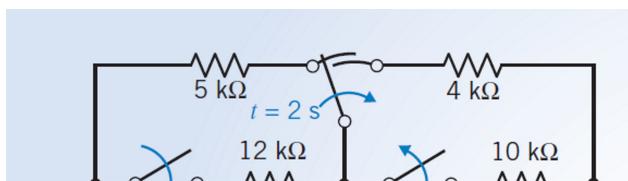
$$\Rightarrow R = \frac{2}{1} = 0.2\text{ }\Omega$$



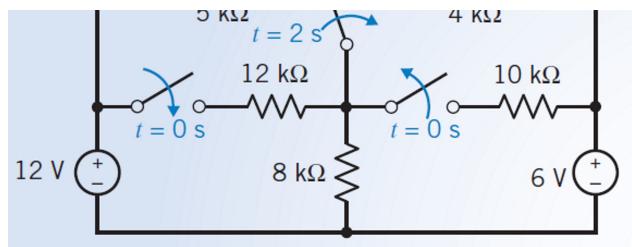


$$\Rightarrow R = \frac{2}{10} = 0.2 \Omega$$


Νόμοι του Kirchhoff:

(KCL) Το άθροισμα των ρευμάτων σε κάθε κόμβο είναι μηδέν

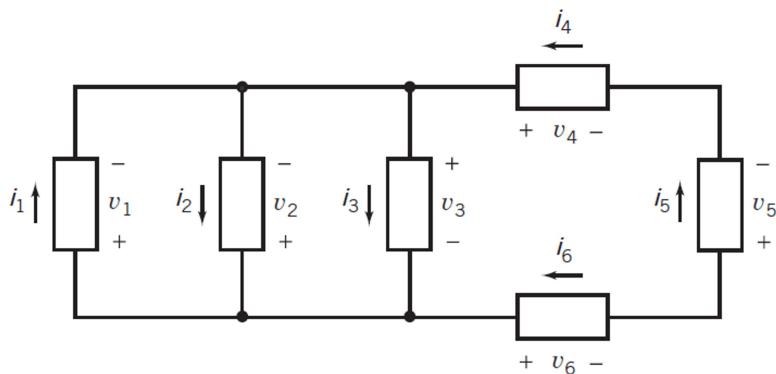(KVL) Το άθροισμα των τάσεων σε κάθε βρόγχο είναι μηδέν



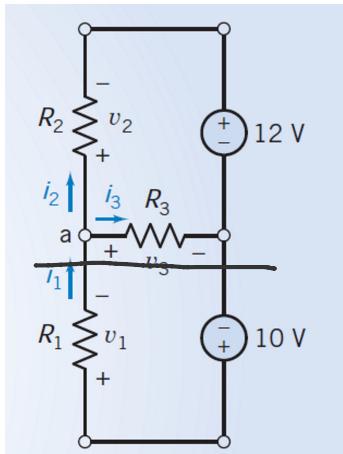
Σε κάθε αντίσταση γνωρίζω ότι $V=RI$ (Ohm)



$$R_1 = 8 \Omega \quad i_3 = 2 A \quad V_2 = -10V$$



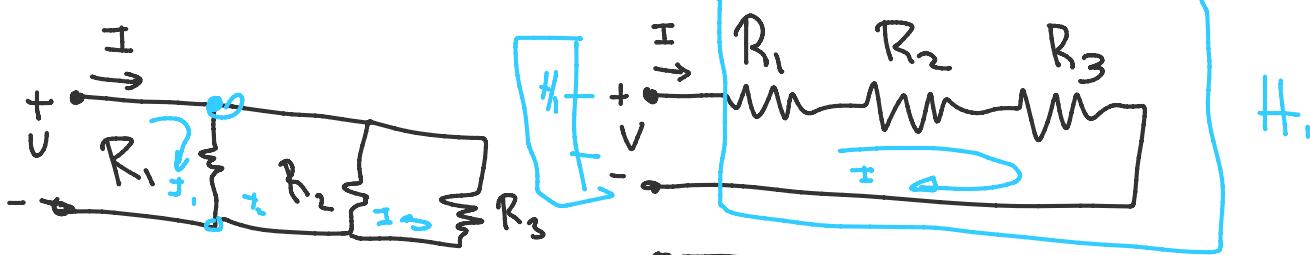Παράλληλη και σε σειρά σύνδεση αντιστάσεων



$$I = I_1 + I_2 + I_3 \Rightarrow R = R_1 + R_2 + R_3$$

$$V = V_{R_1} + V_{R_2} + V_{R_3} = R_1 I + R_2 I + R_3 I \Rightarrow$$

$$V = \underbrace{(R_1 + R_2 + R_3)}_R I$$



$$V = R \cdot I$$

Table 3.5-1 Parallel and Series Voltage and Current Sources

CIRCUIT	EQUIVALENT CIRCUIT	CIRCUIT	EQUIVALENT CIRCUIT
	Not allowed		
			Not allowed


V_{min} V i

Παράδειγμα

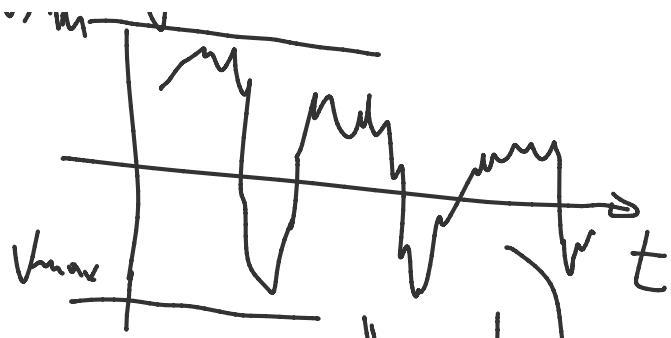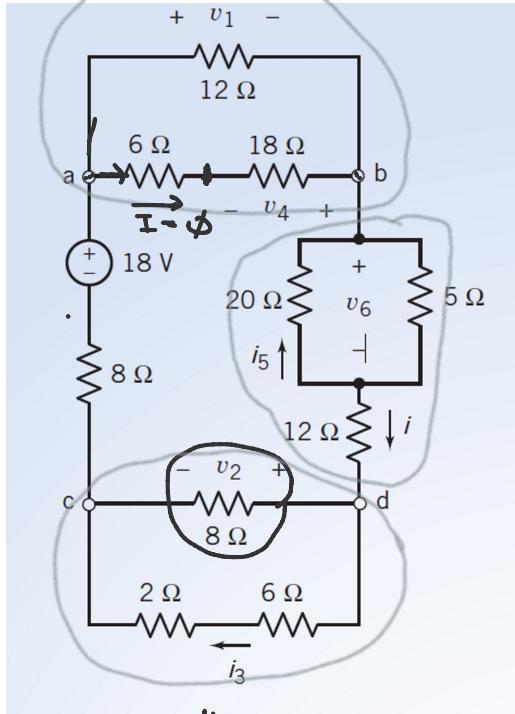

$$V_b - V_d = 3V$$

3.6

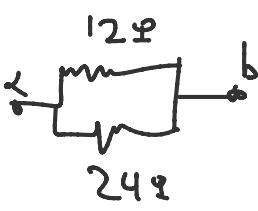

gbit


10bit
 $2^{10} = 1024$
(0, 1023)

$$\frac{1}{R_s} = \frac{1}{12} + \frac{1}{24}$$


$$\frac{3.6V}{1024} \approx 3.6mV$$

$$R_s = \frac{12 \cdot 24}{12+24} = 3.6V$$

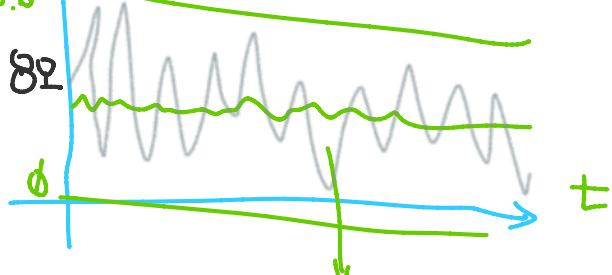
$$= \frac{12 \cdot 8}{36} \cdot 8\Omega$$



$$VR_2 = 16\Omega \times 0.5A = 8V$$

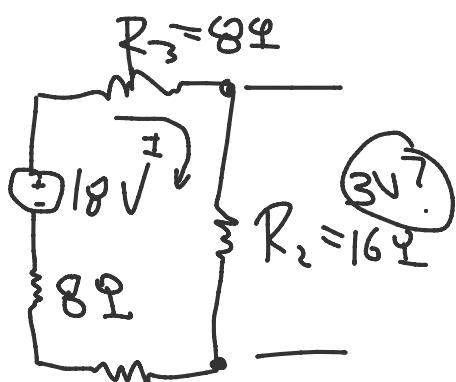



$$R_1 = 4\Omega$$

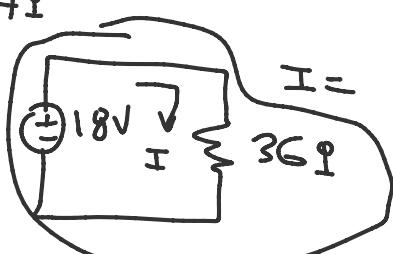


$$\frac{18}{36} = 0.5A$$

$$\Rightarrow I_1 = \frac{3V}{16\Omega} = 0.18A$$

Series resistors

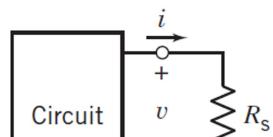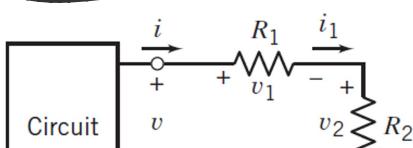


Series resistors

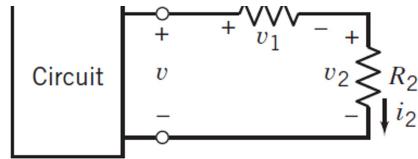

$$i = i_1 = i_2, v_1 = \frac{R_1}{R_1 + R_2} v, \text{ and } v_2 = \frac{R_2}{R_1 + R_2} v$$


:

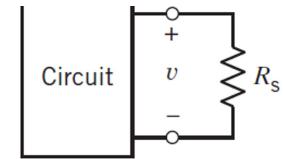


$$R_s = R_1 + R_2 \quad \text{and} \quad v = R_s i$$

$$\hookrightarrow = \frac{S_1 \cdot S_2}{S_1 + S_2}$$

Parallel resistors

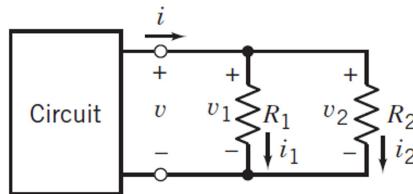

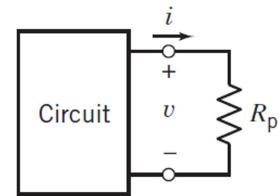
$$v = v_1 = v_2, i_1 = \frac{R_2}{R_1 + R_2} i, \text{ and } i_2 = \frac{R_1}{R_1 + R_2} i$$




$$R_p = \frac{R_1 R_2}{R_1 + R_2} \quad \text{and} \quad v = R_p i$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_p}$$

Series voltage sources

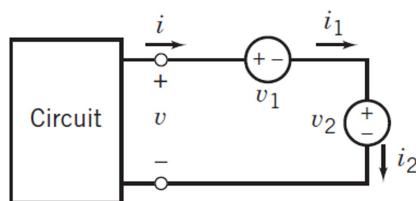

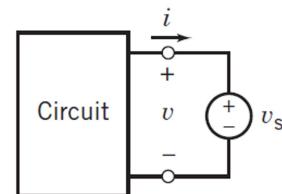
$$i = i_1 = i_2 \quad \text{and} \quad v = v_1 + v_2$$




$$v_s = v_1 + v_2$$

Parallel current sources

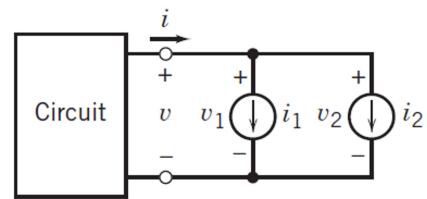
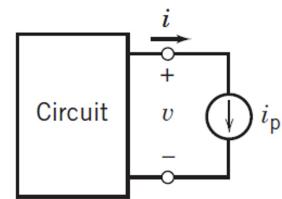
$$v = v_1 = v_2 \quad \text{and} \quad i = i_1 + i_2$$



$$i_p = i_1 + i_2$$